

Digital Design with Verilog

Lecture 3: Review of Sequential Logic Design




Objectives

- Storage Elements
 - Latches/ Flip-Flops
- Design of Sequential Machines
 - Mealy Type / Moore Type
 - State reduction techniques
- Design Examples
 - Counters
 - Shift registers
 - Sequence Detectors

Sequential Circuits

 - Sequential logic includes storage elements.



- The binary information stored in these elements at any given time defines the *state* of the sequential circuit at that time.

Sequential Circuits


- The block diagram demonstrates that
 - *the outputs in a sequential circuit are a function not only of the inputs, but also of the present state of the storage elements.*
 - *The next state of the storage elements is also a function of external inputs and the present state.*
- Thus, **a sequential circuit is specified by a time sequence of inputs, outputs, and internal states .**
- In contrast, the outputs of combinational logic depend only on the present values of the inputs.

Types of Sequential Circuits

- There are two main types of sequential circuits, and their classification is a function of the timing of their signals.
- A *synchronous* sequential circuit is a system whose behavior can be defined from the knowledge of its signals at discrete instants of time.
- The behavior of an *asynchronous* sequential circuit depends upon the input signals at any instant of time *and* the order in which the inputs change.

Synchronous Sequential Logic

 - The storage elements (memory) used in clocked sequential circuits are called *flip-flops*.
- A flip-flop is a binary storage device capable of storing one bit of information.
 - In a stable state, the output of a flip-flop is either 0 or 1.



(a) Block diagram




(b) Timing diagram of clock pulses



Storage Elements: Latches and Flip-Flops

- Storage elements that operate with signal levels (rather than signal transitions) are referred to as *latches*; those controlled by a clock transition are *flip-flops*.
- Latches are said to be level sensitive devices; flip-flops are edge-sensitive devices.
- The two types of storage elements are related because latches are the basic circuits from which all flip-flops are constructed.

SR Latch

 


(a) Logic diagram

S	R	Q	Q'
1	0	1	0
0	0	1	0 (after $S = 1, R = 0$)
0	1	0	1
0	0	0	1 (after $S = 0, R = 1$)
1	1	0	0 (forbidden)

(b) Function table

- Under normal conditions, both inputs of the latch remain at 0 unless the state has to be changed.
- The application of a momentary 1 to the S input causes the latch to go to the set state.
- The S input must go back to 0 before any other changes take place.

SR Latch

 


(a) Logic diagram

S	R	Q	Q'
1	0	1	0
0	0	1	0 (after $S = 1, R = 0$)
0	1	0	1
0	0	0	1 (after $S = 0, R = 1$)
1	1	0	0 (forbidden)

(b) Function table

- After both inputs return to 0, it is then possible to shift to the reset state by momentarily applying a 1 to the R input. The 1 can then be removed from R , where upon the circuit remains in the reset state.
- *Thus, when both inputs S and R are equal to 0, the latch can be in either the set or the reset state, depending on which input was most recently a 1.*

SR Latch / S'R' Latch

 


S	R	Q	Q'
1	0	0	1
1	1	0	1 (after $S = 1, R = 0$)
0	1	1	0
1	1	1	0 (after $S = 0, R = 1$)
0	0	1	1 (forbidden)

(b) Function table

- SR latch with NAND gates requires a 0 signal to change its state.
- The inputs signals for the NAND-latch are the complement values used for the NOR latch.

SR Latch with control input

 


(a) Logic diagram

En	S	R	Next state of Q
0	X	X	No change
1	0	0	No change
1	0	1	$Q = 0$; reset state
1	1	0	$Q = 1$; set state
1	1	1	Indeterminate

(b) Function table

- The outputs of the NAND gates stay at the logic-1 level as long as the enable signal remains at 0.

D Latch (Transparent Latch)

 

(a) Logic diagram

En	D	Next state of Q
0	X	No change
1	0	$Q = 0$; reset state
1	1	$Q = 1$; set state




(b) Function table

- *How is D-latch structurally different than the SR latch?*
- D latch eliminates the undesirable condition of the indeterminate state that occurs in the SR latch ($Q = Q' = 1$).

If $D = 1$, $Q = 1$ -> 'set' state

If $D = 0$, $Q = 0$ -> 'reset' state


Graphic Symbols for Latches

   

Flip-Flops


- A flip-flop is a state of a latch that can be switched by momentary change in the control input.
- This momentary change is called a trigger and the transition it causes is said to trigger the flip-flop.
- The *D*-latch is a flip-flop that is triggered every time the pulse goes to a high or logic level 1.

Edge-Triggered Flip-Flop

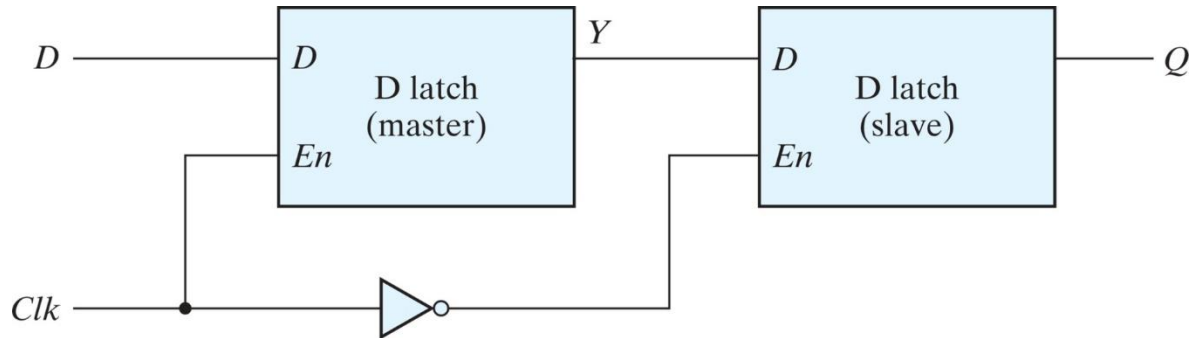


- The circuit samples the D input and changes its output at the negative edge of the clock, Clk .
- When the clock is 0, the output of the inverter is 1. The slave latch is enabled and its output Q is equal to the master output Y . The master latch is disabled ($Clk = 0$).
- When the Clk changes to high, D input is transferred to the master latch. The slave remains disabled as long as En is low. Any change in the input changes Y , but not Q .
- The output of the flip-flop can change when CLK makes a transition $1 \rightarrow 0$

 Edge-Triggered Flip-Flop: Graphic Symbols




(a) Positive-edge

 

(a) Negative-edge


- The most economical and efficient flip-flop constructed is the edge-triggered D flip-flop since it requires the smallest number of gates.

CMOS Master Slave Circuit

 


CMOS master–slave circuit of a D-type flip-flop: circuit schematic

CMOS Master Slave Circuit

 


Timing definitions for D, Clk, and Q waveforms.

JK Flip-Flop

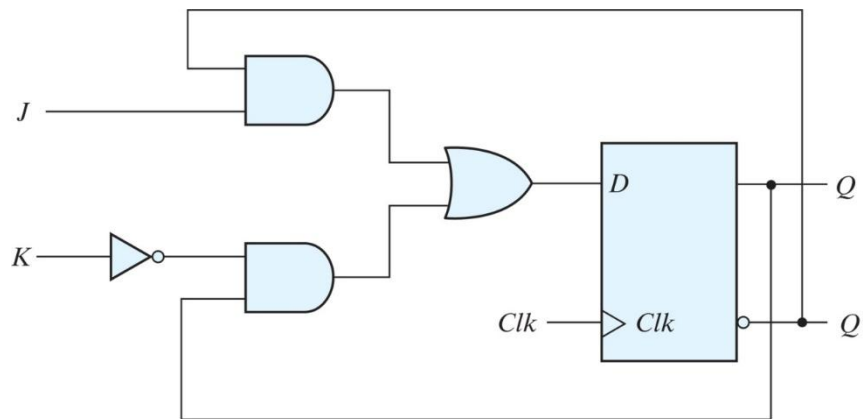


(a) Circuit diagram

 

(b) Graphic symbol

- When $J = 1$ and $K = 0$, $D = 1 \rightarrow$ next clock edge sets output to 1.
- When $J = 0$ and $K = 1$, $D = 0 \rightarrow$ next clock edge resets output to 0.
- When $J = 1$ and $K = 1$, $D = Q' \rightarrow$ next clock edge complements output.
- When $J = 0$ and $K = 0$, $D = Q \rightarrow$ next clock edge leaves output unchanged.

T Flip-Flop

 

- The T (toggle) flip-flop is a complementing flip-flop and can be obtained from a JK flip-flop when inputs J and K are tied together.
- When $T = 0$ ($J = K = 0$), a clock edge does not change the output. When $T = 1$ ($J = K = 1$), a clock edge complements the output.
- The T flip-flop can also be constructed with a D flip-flop and an exclusive-OR gate.



Characteristic Tables and Equations

Flip-Flop Characteristic Tables

JK Flip-Flop

<i>J</i>	<i>K</i>	<i>Q (t + 1)</i>	
0	0	$Q(t)$	No change
0	1	0	Reset
1	0	1	Set
1	1	$Q'(t)$	Complement





D Flip-Flop

<i>D</i>	<i>Q (t + 1)</i>	
0	0	Reset
1	1	Set

T Flip-Flop



<i>T</i>	<i>Q (t + 1)</i>	
0	$Q(t)$	No change
1	$Q'(t)$	Complement

Excitation Tables

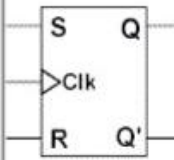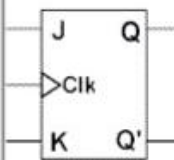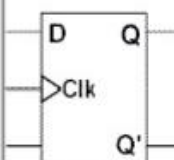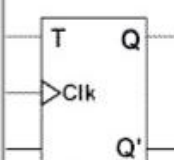FLIP-FLOP NAME	FLIP-FLOP SYMBOL	CHARACTERISTIC TABLE	CHARACTERISTIC EQUATION	EXCITATION TABLE																																			
SR		<table><tr><th>S</th><th>R</th><th>Q(next)</th></tr><tr><td>0</td><td>0</td><td>Q</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>?</td></tr></table>	S	R	Q(next)	0	0	Q	0	1	0	1	0	1	1	1	?	$Q_{(next)} = S + R'Q$ $SR = 0$	<table><tr><th>Q</th><th>Q(next)</th><th>S</th><th>R</th></tr><tr><td>0</td><td>0</td><td>0</td><td>X</td></tr><tr><td>0</td><td>1</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>X</td><td>0</td></tr></table>	Q	Q(next)	S	R	0	0	0	X	0	1	1	0	1	0	0	1	1	1	X	0
S	R	Q(next)																																					
0	0	Q																																					
0	1	0																																					
1	0	1																																					
1	1	?																																					
Q	Q(next)	S	R																																				
0	0	0	X																																				
0	1	1	0																																				
1	0	0	1																																				
1	1	X	0																																				
JK		<table><tr><th>J</th><th>K</th><th>Q(next)</th></tr><tr><td>0</td><td>0</td><td>Q</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>Q'</td></tr></table>	J	K	Q(next)	0	0	Q	0	1	0	1	0	1	1	1	Q'	$Q_{(next)} = JQ' + K'Q$	<table><tr><th>Q</th><th>Q(next)</th><th>J</th><th>K</th></tr><tr><td>0</td><td>0</td><td>0</td><td>X</td></tr><tr><td>0</td><td>1</td><td>1</td><td>X</td></tr><tr><td>1</td><td>0</td><td>X</td><td>1</td></tr><tr><td>1</td><td>1</td><td>X</td><td>0</td></tr></table>	Q	Q(next)	J	K	0	0	0	X	0	1	1	X	1	0	X	1	1	1	X	0
J	K	Q(next)																																					
0	0	Q																																					
0	1	0																																					
1	0	1																																					
1	1	Q'																																					
Q	Q(next)	J	K																																				
0	0	0	X																																				
0	1	1	X																																				
1	0	X	1																																				
1	1	X	0																																				
D		<table><tr><th>D</th><th>Q(next)</th></tr><tr><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td></tr></table>	D	Q(next)	0	0	1	1	$Q_{(next)} = D$	<table><tr><th>Q</th><th>Q(next)</th><th>D</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	Q	Q(next)	D	0	0	0	0	1	1	1	0	0	1	1	1														
D	Q(next)																																						
0	0																																						
1	1																																						
Q	Q(next)	D																																					
0	0	0																																					
0	1	1																																					
1	0	0																																					
1	1	1																																					
T		<table><tr><th>T</th><th>Q(next)</th></tr><tr><td>0</td><td>Q</td></tr><tr><td>1</td><td>Q'</td></tr></table>	T	Q(next)	0	Q	1	Q'	$Q_{(next)} = TQ' + T'Q$	<table><tr><th>Q</th><th>Q(next)</th><th>T</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	Q	Q(next)	T	0	0	0	0	1	1	1	0	1	1	1	0														
T	Q(next)																																						
0	Q																																						
1	Q'																																						
Q	Q(next)	T																																					
0	0	0																																					
0	1	1																																					
1	0	1																																					
1	1	0																																					

Mealy and Moore Models of FSMs

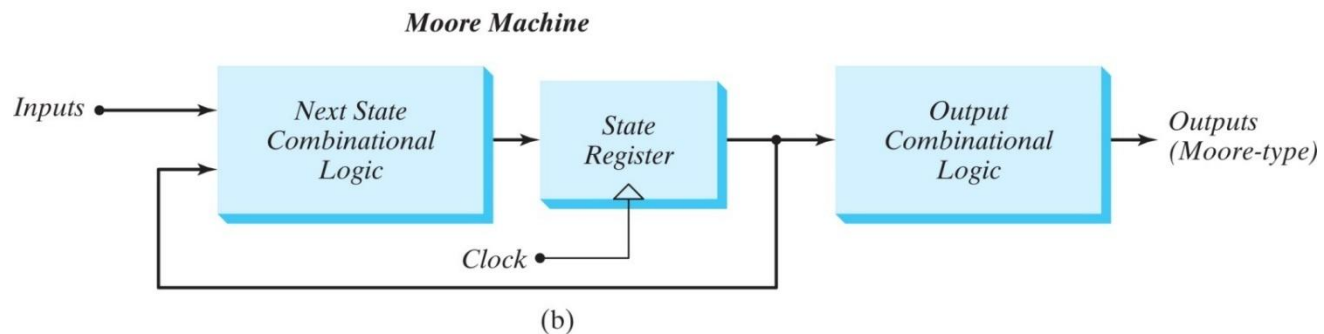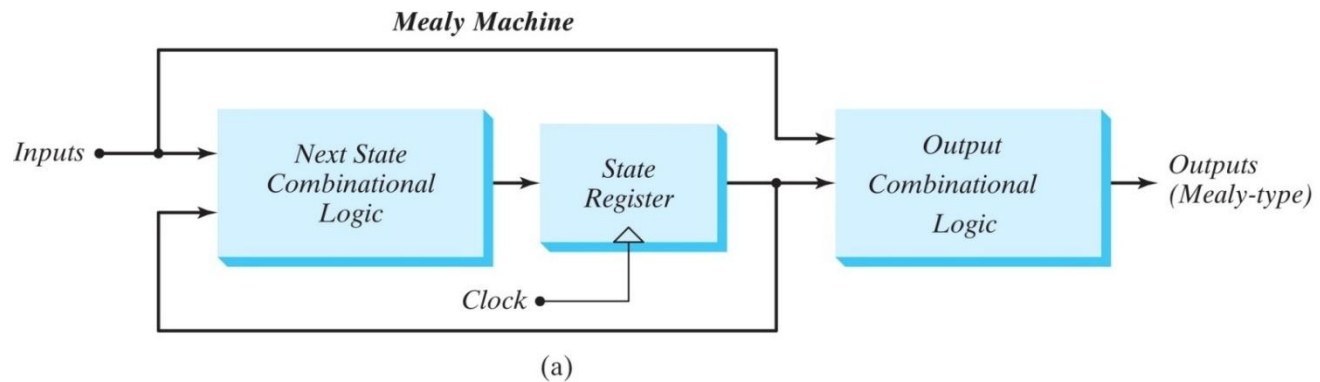- **Mealy model**, the output is a function of both the present state and the input.
- **Moore model**, the output is a function of only present state




State Reduction and Equivalent States

State Reduction and Equivalent States

- Two states of a sequential machine are equivalent (\equiv) if they have the **same output sequence** for **all possible input sequences**.
- Such states of the machine cannot be distinguished from each other based on observed outputs.
- Equivalent states can be combined without changing the input-output behavior of the machine.
 - Leads to a reduction in hardware without compromising functionality

Example: State Reduction

 


Note that we use letters to designate the states for the time being

Example: State Reduction

state	a	a	b	c	f	g	f	f	g	a	a		
input	0	1	0	1	0	1	1	0	0	0	0		
output	0	0	0	0	0	1	1	0	0	0			

- What is important
 - not the states
 - but the output values the circuit generates
- Therefore, the problem is to find a circuit
 - with fewer number of states,
 - but that produces the same output pattern for any given input pattern, starting with the same initial state

State Reduction Technique 1/7

 

- Step 1: get **a** state table

present state	next state		Output	
	x = 0	x = 1	x = 0	x = 1
a	a	b	0	0
b	c	d	0	0
c	c	f	0	0
d	e	f	0	1
e	a	f	0	1
f	g	f	0	1
g	a	f	0	1

State Reduction Technique 2/7

- Step 2: Inspect the state table for equivalent states
 - Equivalent states: Two states,
 1. that produce the same output
 2. whose next states are identicalfor each input combination

State Reduction Technique 3/7

present state	next state		Output	
	x = 0	x = 1	x = 0	x = 1
a	a	b	0	0
b	c	d	0	0
c	c	f	0	0
d	e	f	0	1
e	a	f	0	1
f	g	f	0	1
g	a	f	0	1

- States “e” and “g” are equivalent
- One of them can be removed

State Reduction Technique 4/7

present state	next state		Output	
	x = 0	x = 1	x = 0	x = 1
a	a	b	0	0
b	c	d	0	0
c	c	f	0	0
d	e	f	0	1
e	a	f	0	1
f	e	f	0	1

- We keep looking for equivalent states

State Reduction Technique 5/7

present state	next state		Output	
	x = 0	x = 1	x = 0	x = 1
a	a	b	0	0
b	c	d	0	0
c	c	d	0	0
d	e	d	0	1
e	a	d	0	1


- We keep looking for equivalent states

State Reduction Technique 6/7

present state	next state		Output	
	x = 0	x = 1	x = 0	x = 1
a	a	b	0	0
b	b	d	0	0
d	e	d	0	1
e	a	d	0	1

- We stop when there are no equivalent states

State Reduction Technique 7/7

 

present state	next state		Output	
	x = 0	x = 1	x = 0	x = 1
a	a	b	0	0
b	b	d	0	0
d	e	d	0	1
e	a	d	0	1


We need two flip-flops

state	a	a	b	b	d	e	d	d	e	d	e		
input	0	1	0	1	0	1	1	0	1	0	0		
output	0	0	0	0	0	1	1	0	0	0	0		

Counters


Asynchronous (Ripple) Counters

 - Example: 2-bit ripple binary counter.
- Output of one flip-flop is connected to the clock input of the next more-significant flip-flop.





Asynchronous (Ripple) Counters

- Example: 3-bit ripple binary counter.

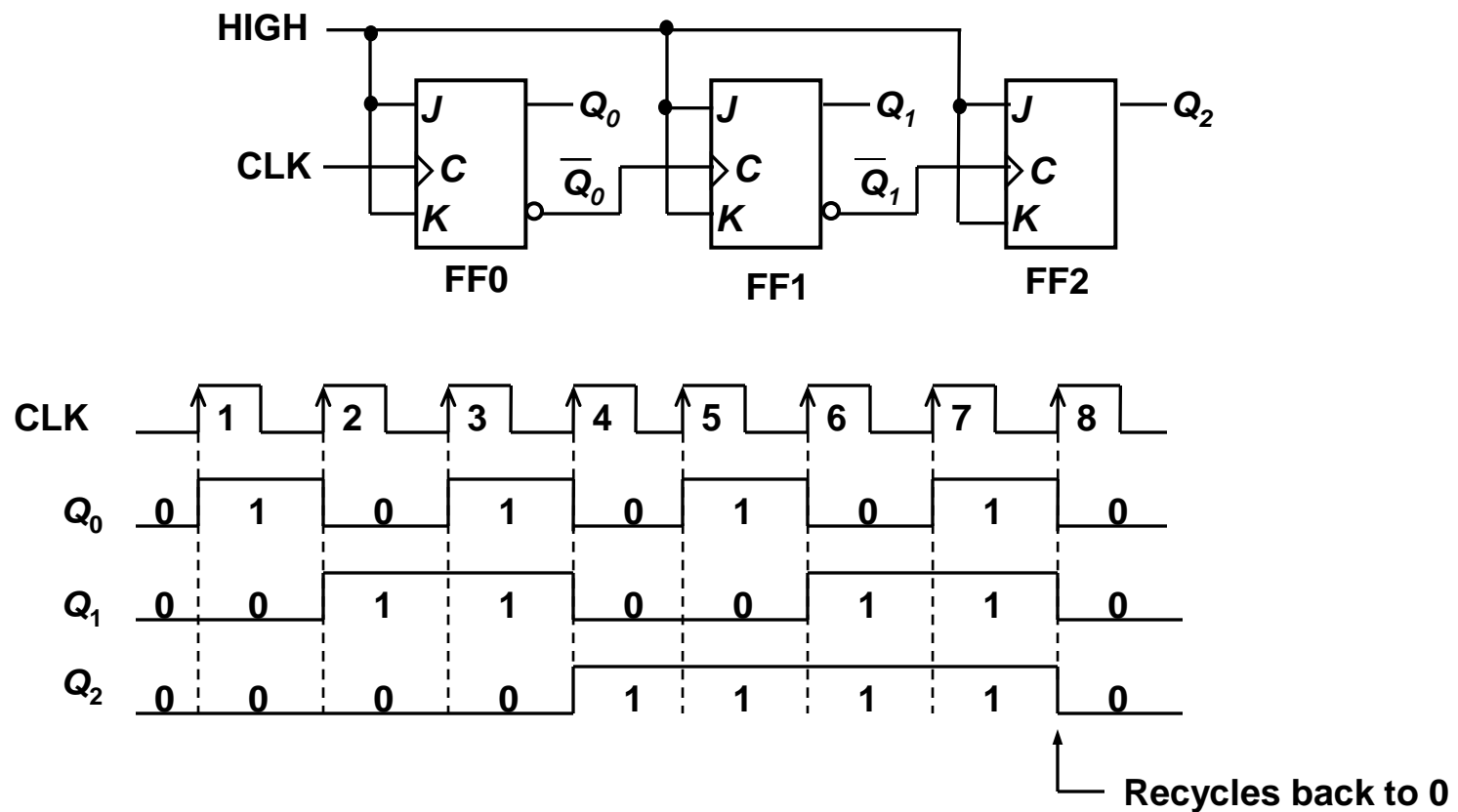


Asyn. Counters with MOD no. $< 2^n$

  - Asynchronous decade/BCD counter (cont'd).




Asynchronous Down Counters

 - So far we are dealing with up counters. Down counters, on the other hand, count downward from a maximum value to zero, and repeat.
- Example: A 3-bit binary (MOD-8) down counter.




3-bit binary
up counter

 

3-bit binary
down counter

Asynchronous Down Counters

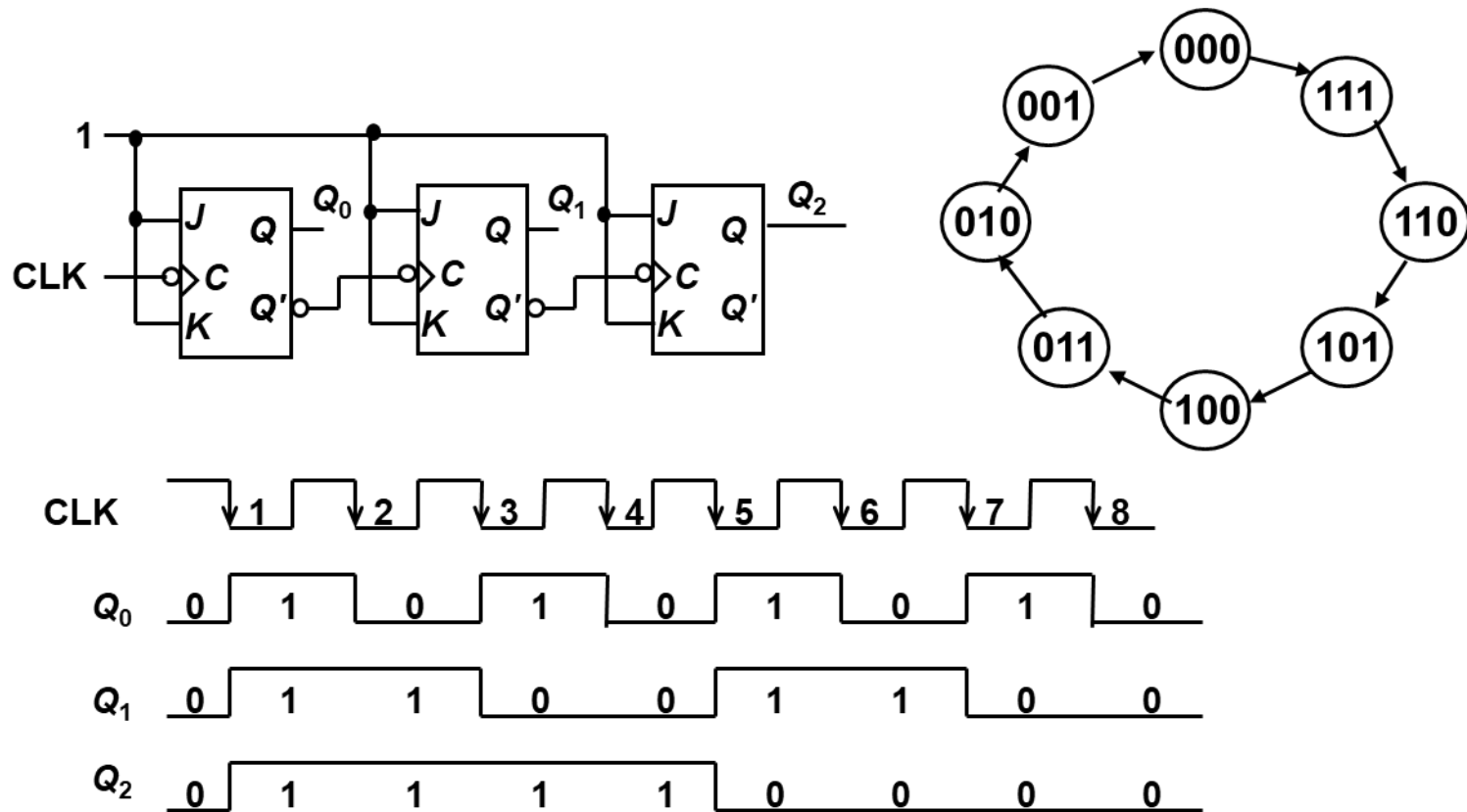
- Example: A 3-bit binary (MOD-8) down counter.




Synchronous Counters

- Example: 3-bit synchronous binary counter (using T flip-flops, or JK flip-flops with identical J, K inputs).


Present state			Next state			Flip-flop inputs		
A_2	A_1	A_0	A_2^+	A_1^+	A_0^+	TA_2	TA_1	TA_0
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	0	1
1	1	1	0	0	0	1	1	1

 

$$TA_2 = A_1 \cdot A_0$$

 

$$TA_1 = A_0$$

 

$$TA_0 = 1$$


Synchronous Counters

- Example: 3-bit synchronous binary counter (cont'd).

$$TA_2 = A_1.A_0$$

$$TA_1 = A_0$$

$$TA_0 = 1$$

 

Up/Down Synchronous Counters

- Example: A 3-bit up/down synchronous binary counter.

Clock pulse	<i>Up</i>	Q_2	Q_1	Q_0	<i>Down</i>
0	↻	0	0	0	↻
1	↻	0	0	1	↻
2	↻	0	1	0	↻
3	↻	0	1	1	↻
4	↻	1	0	0	↻
5	↻	1	0	1	↻
6	↻	1	1	0	↻
7	↻	1	1	1	↻

$$TQ_0 = 1$$

$$TQ_1 = (Q_0 \cdot Up) + (Q_0' \cdot Up')$$

$$TQ_2 = (Q_0 \cdot Q_1 \cdot Up) + (Q_0' \cdot Q_1' \cdot Up')$$

Up counter

$$TQ_0 = 1$$

$$TQ_1 = Q_0$$

$$TQ_2 = Q_0 \cdot Q_1$$



Down counter

$$TQ_0 = 1$$

$$TQ_1 = Q_0'$$


$$TQ_2 = Q_0' \cdot Q_1'$$

Counters with Parallel Load

  


Clear	CLK	Load	Count	Function
0	X	X	X	Clear to 0
1	↑	1	X	Load inputs
1	↑	0	1	Count next binary state
1	↑	0	0	No change

Counters with Parallel Load

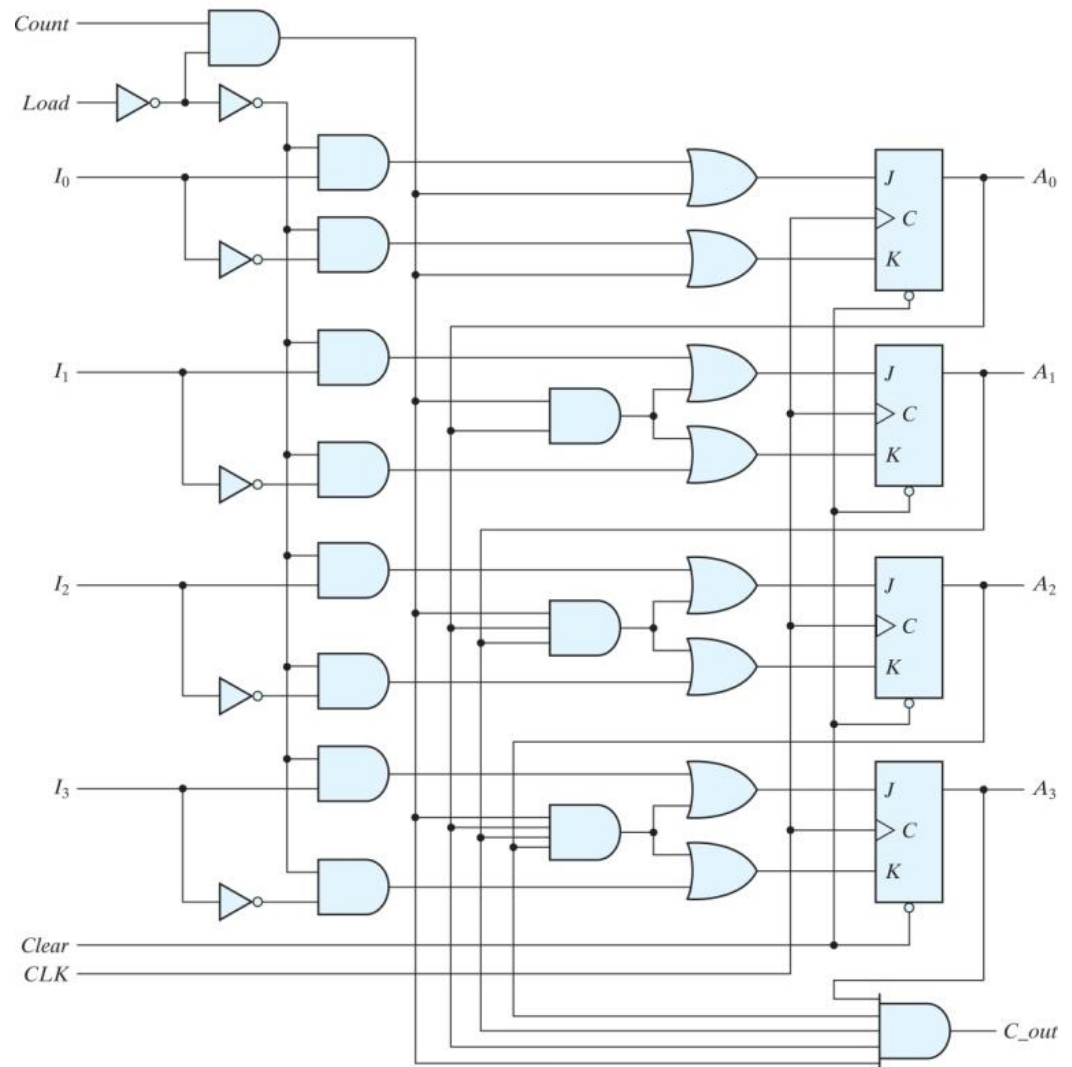

Cascading Synchronous Counters

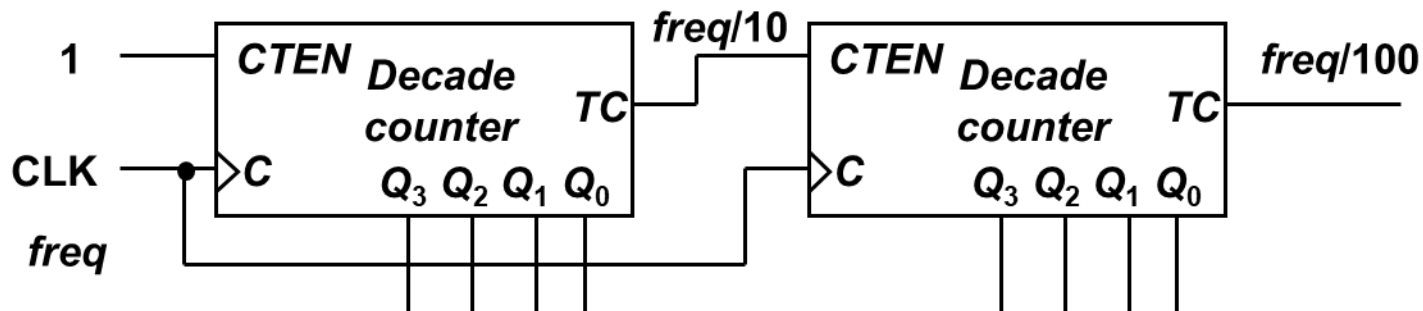- If counter is not a binary counter, requires additional output.
- Example: A modulus-100 counter using two-decade counters.




$TC = 1$ when counter recycles to 0000

- **CTEN**---Counter Enable, **TC**= Terminal Count

Shift Registers

Shift Registers

- Basic data movement in shift registers

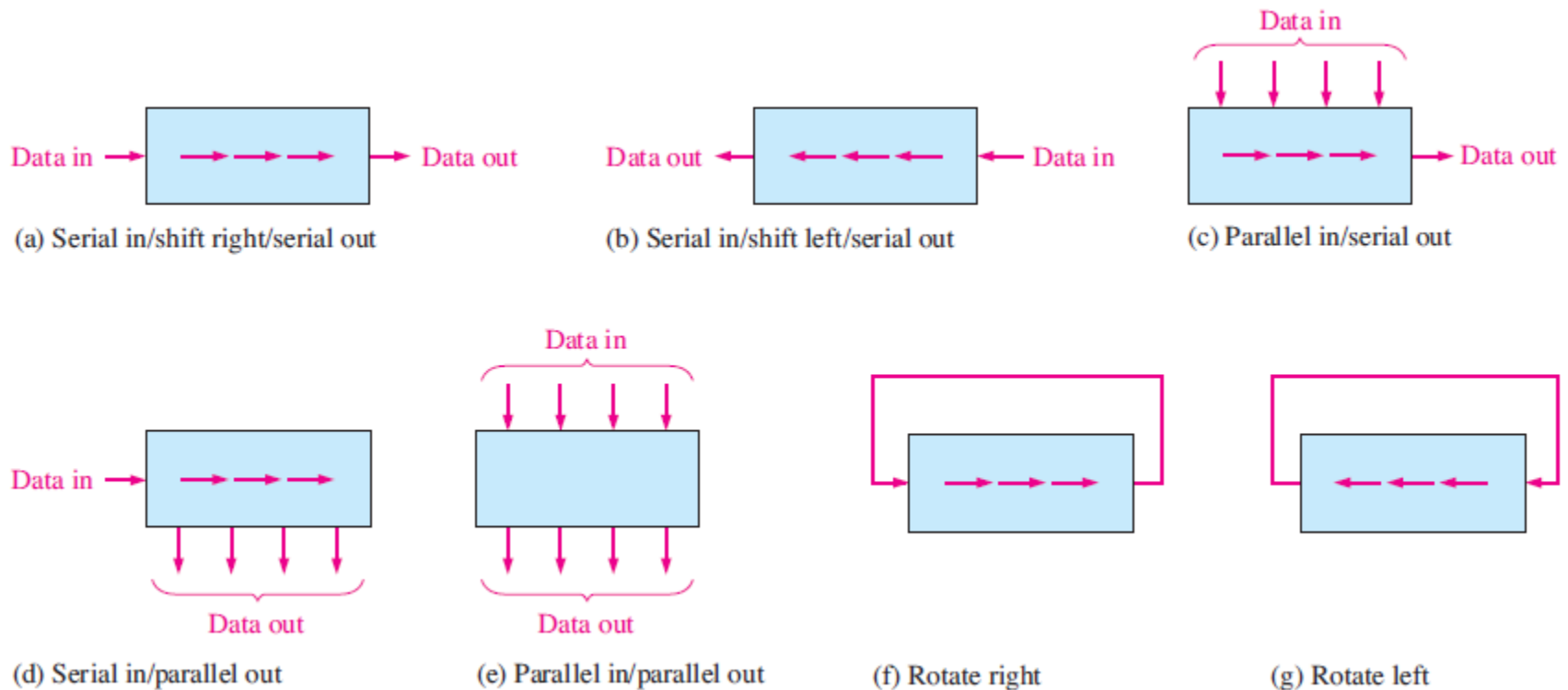

Serial In/Serial Out Shift Registers

- Accepts data serially – one bit at a time – and also produces output serially.



 


FIGURE 8–3 Serial in/serial out shift register.

 

Bidirectional Shift Registers

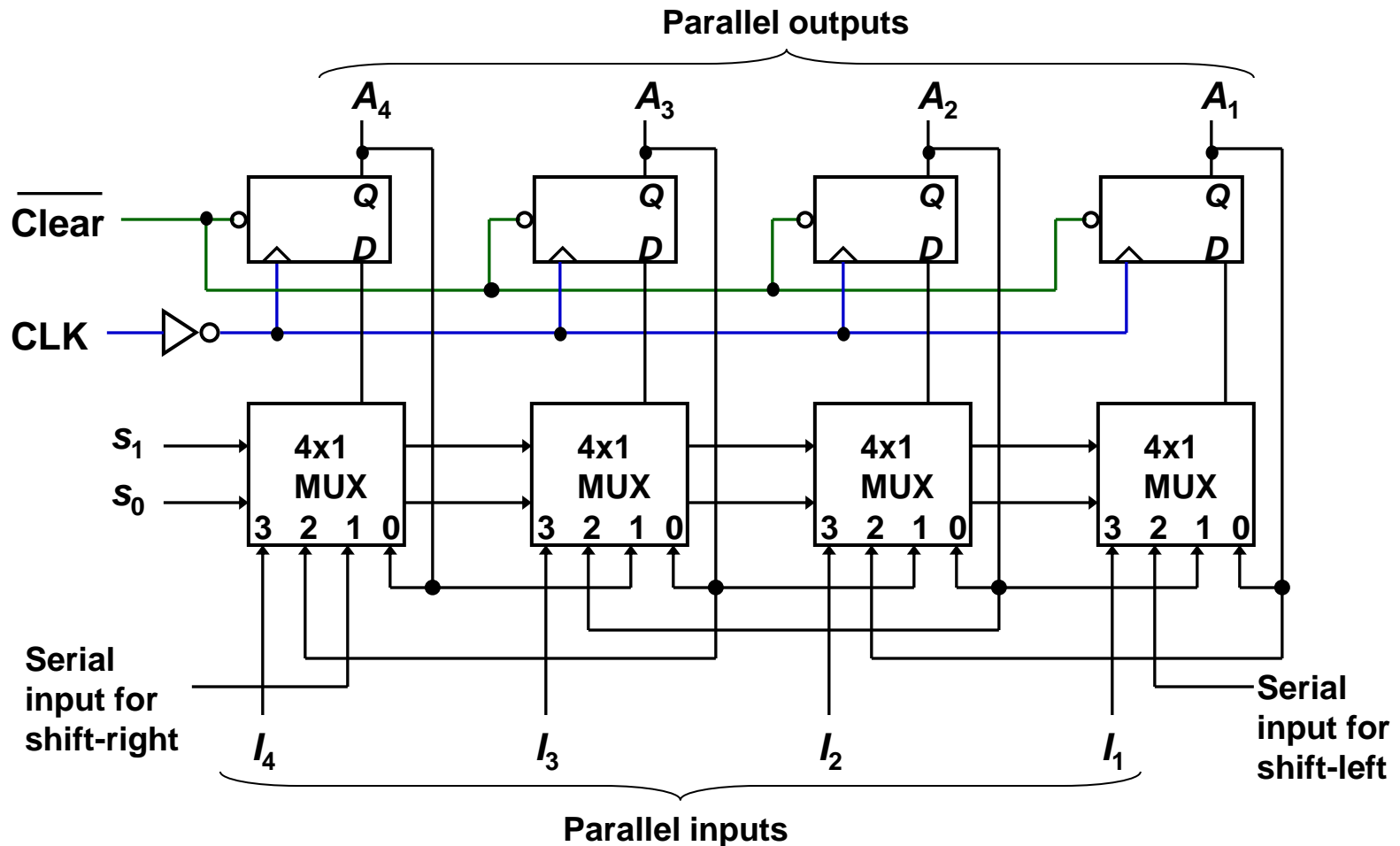- 4-bit bidirectional shift register with parallel load.



Bidirectional Shift Registers


- 4-bit bidirectional shift register with parallel load.

<i>Mode Control</i>		<i>Register Operation</i>
<i>s₁</i>	<i>s₀</i>	
0	0	No change
0	1	Shift right
1	0	Shift left
1	1	Parallel load

An Application – Serial Addition

- Most operations in digital computers are done in parallel. Serial operations are slower but require less equipment.
- A serial adder is shown below.

$$A \leftarrow A + B.$$

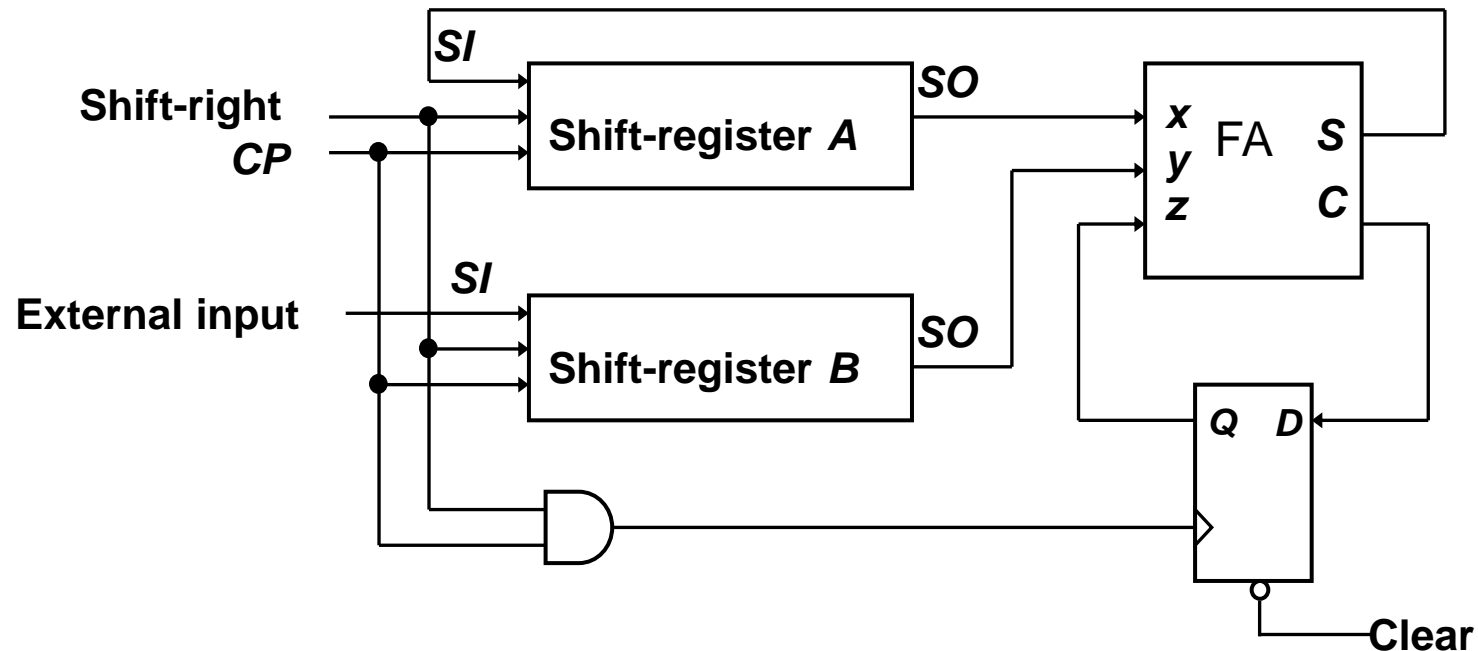

Sequence Detectors

Sequence Detector

- Mealy machine, 101 sequence
- For non overlapping case


Input :0110101011001
Output:0000100010000

- For overlapping case

Input: 0110101011001
Output: 0000101010000

Sequence Detector


- 101 sequence Detector

 

X	=	0	0	1	1	0	1	1	0	0	1	0	1	0	1	0	0
Z	=	0	0	0	0	0	1	0	0	0	0	0	1	0	1	0	0
(time:		0	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15)


Design of 101 Sequence Detector (Mealy)

- State Diagram:

 

Design of 101 Sequence Detector


- State Diagram (final):

 

Design of 101 Sequence Detector

- State Table:

Present state	Next State		Present Output	
	X = 0	X = 1	X = 0	X = 1
S ₀	S ₀	S ₁	0	0
S ₁	S ₂	S ₁	0	0
S ₂	S ₀	S ₁	0	1

 

- State Table with State Assignment:

AB	A ⁺ B ⁺		Z	
	X = 0	X = 1	X = 0	X = 1
00	00	01	0	0
01	10	01	0	0
10	00	01	0	1

Design of 101 Sequence Detector

- Derive Boolean Equations:

X \ A B	A			
	00	01	11	10
0	0	1	X	0
1	0	0	X	0

B

$$D_A = X'.B$$

X \ A B	A			
	00	01	11	10
0	0	0	X	0
1	1	1	X	1

B


$$D_B = X$$

X \ A B	A			
	00	01	11	10
0	0	0	X	0
1	0	0	X	1


B

$$Z = X.A$$

Design of Sequence Detector

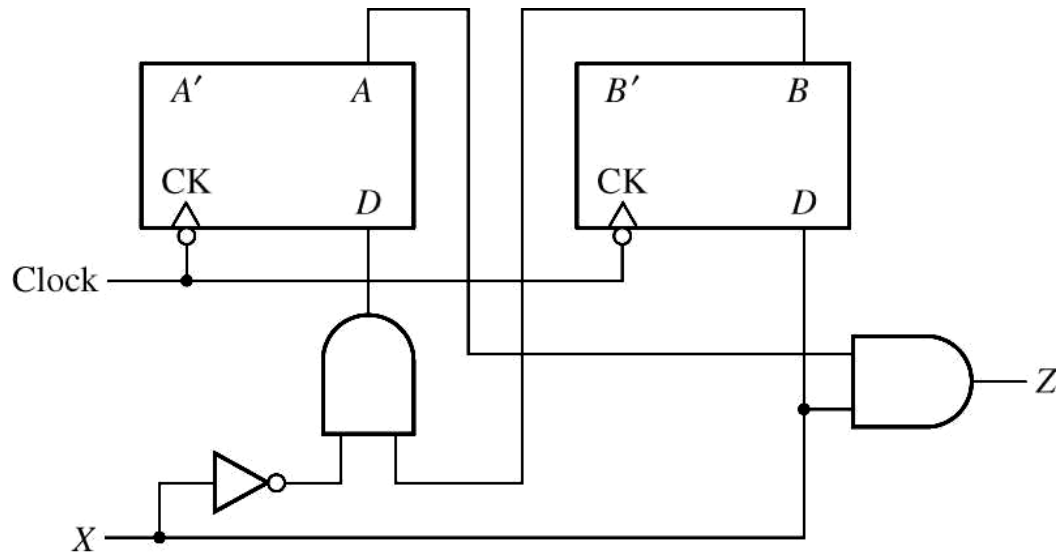


Compare with Typical Mealy Machine

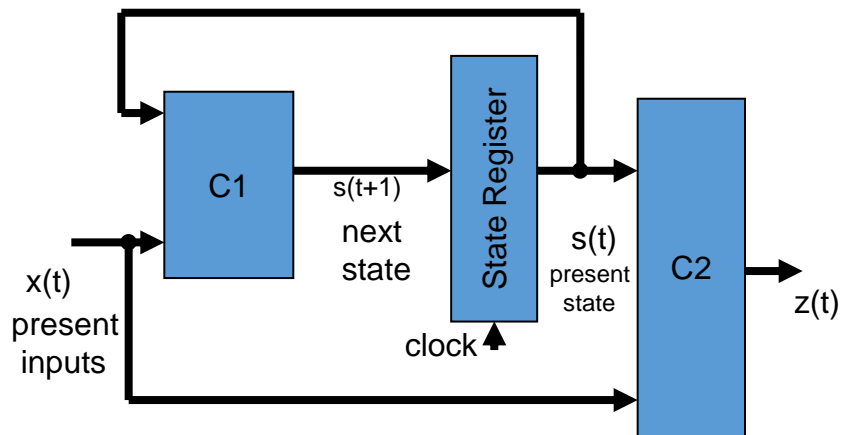


Design of Sequence Detector

- A Moore Sequence Detector:

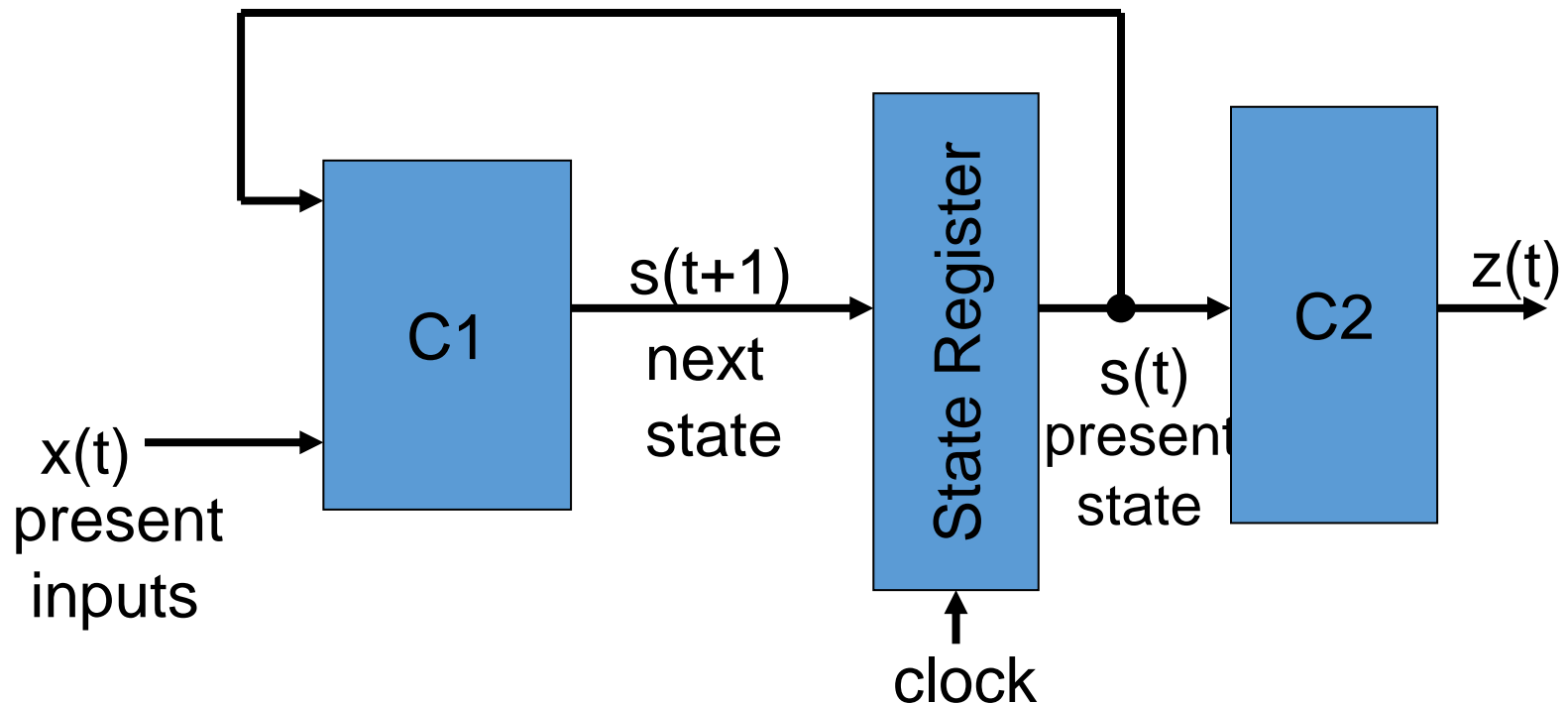

Sequence Detector

- 101 sequence Detector

 

X	=	0	0	1	1	0	1	1	0	0	1	0	1	0	1	0	0
Z	=	0	0	0	0	0	1	0	0	0	0	0	1	0	1	0	0
(time:		0	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15)



Design of a Sequence Detector

S_0 : start

S_1 : got 1

S_2 : got 10

S_3 : got 101

  


Design of a Sequence Detector

S_0 : start

S_1 : got 1

S_2 : got 10

S_3 : got 101

 

Design of a Sequence Detector

- State Table

Present state	Next State		Present Output (Z)
	X = 0	X = 1	
S ₀	S ₀	S ₁	0
S ₁	S ₂	S ₁	0
S ₂	S ₀	S ₃	0
S ₃	S ₂	S ₁	1

- Transition Table with State assignment

AB	D _A D _B A ⁺ B ⁺		Z
	X = 0	X = 1	
00	00	01	0
01	11	01	0
11	00	10	0
10	11	01	1

Design of a Sequence Detector

		A B		A	
		00	01	11	10
X	0	0	1	0	1
	1	0	0	1	0

B

$$D_A = \bar{X}\bar{A}B + XAB + \bar{X}A\bar{B}$$

		A B		A	
		00	01	11	10
X	0	0	1	0	1
	1	1	1	0	1

B

$$D_B = \bar{A}B + X\bar{B} + A\bar{B}$$

$$Z = A\bar{B}$$

References

- Chapter 9, Digital Fundamentals by Thomas L. Floyd
- Chapter 5 & 6, Digital Design by M. Morris Mano
- Disclaimer: I don't own all the slides, few of these slides are copied and adopted from various public resources available on the internet.

Thank you