

Digital Design with Verilog

Verilog

Lecture 16: Data path and Control path Design





Complete the quote

“Good artists copy.
Great artists steal.”

-Pablo Picasso

- The following slides are only slightly modified from those in the MIT 6.375 course, Prof. Arvind
<http://csg.csail.mit.edu/6.375/>
- Verilog Tutorial, by Dr. Sat Garcia [University of San Diego](#).
- Datapath Design, Coding Standards by Michael B.Taylor, UCSD.



Learning Objectives

- Data path & Control path
- Separating control from data
- Designing Data path
- Designing Control path
- Integrating Data path & Control path



Data Path


- The datapath is where data moves from place to place.
 - Computation happens in the datapath
 - No decisions are made here.
 - Things you should find in a datapath
 - Muxes
 - Registers
 - ALUs
 - Mostly about wiring things up



Control Path

- Control is where decisions are made
- Things you will find there are
 - State machines
 - Random lots of complex logic
 - Little state (maybe just a single register)
- There are best practices from people who build real chips---Following them will save you lots of pain.

Basic Design

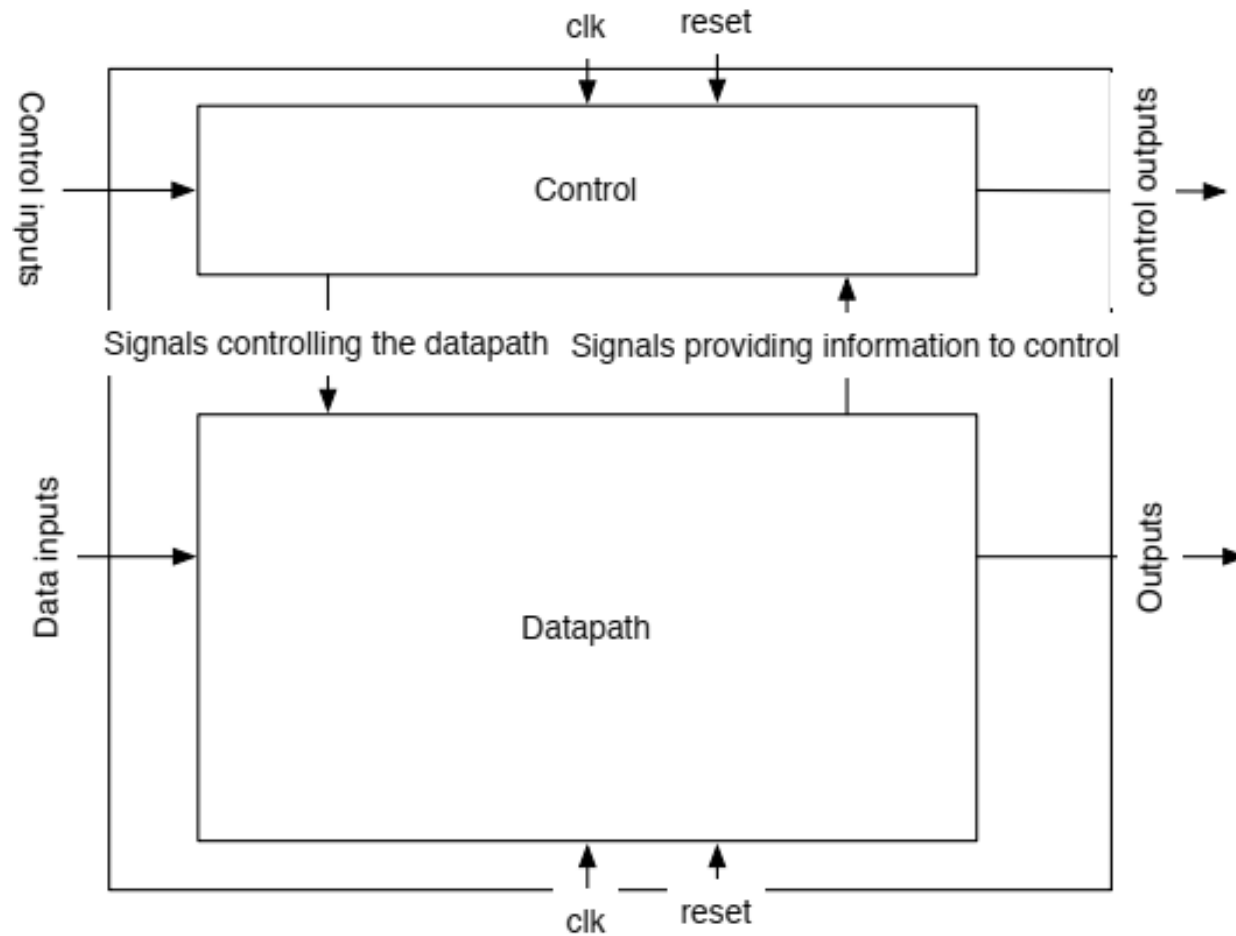



Designing a GCD Calculator

Euclid's algorithm for computing the Greatest Common Divisor (GCD):

15	6	
9	6	<i>subtract</i>
3	6	<i>subtract</i>
6	3	<i>swap</i>
3	3	<i>subtract</i>
0	<i>answer:</i> 3	<i>subtract</i>



Euclid's algorithm in C

```
int GCD( int inA, int inB) {  
    int done = 0;  
    int A = inA;  
    int B = inB;  
    while ( !done ) {  
        if ( A < B ) {  
            swap = A;  
            A = B;  
            B = swap;  
        }  
        else if ( B != 0 )  
            A = A - B;  
        else  
            done = 1;  
    }  
    return A;  
}
```

How do we implement
this in hardware?



Greatest Common Divisor

```
module gcd_beh #( parameter W = 16 ) (  
    input [W-1:0] inA, inB,  
    output [W-1:0] out);  
  
    reg [W-1:0] A, B, out, swap;  
    integer done;  
  
    always @(*)  
    begin  
        done = 0;  
        A = inA;  
        B = inB;  
        while (!done)  
        begin  
            if ( A < B )  
            begin  
                swap = A;  
                A = B;  
                B = swap;  
            end  
            else if ( B!=0 )  
                A=A-B;  
            else  
                done = 1;  
            end  
            out = A;  
        end  
    end  
endmodule
```



Greatest Common Divisor

```
module gcd_beh_tb;
    reg [15:0] inA, inB;
    wire [15:0] out;
    gcd_beh#(16) gcd_unit( .inA(inA), .inB(inB), .out(out) );
    initial
    begin
        // 3 = GCD( 27, 15 )
        inA = 27;
        inB = 15;
        #10;
        if ( out == 3 )
            $display( "Test ( gcd(27,15) ) succeeded, [ %x == %x ]", out, 3 );
        else
            $display( "Test ( gcd(27,15) ) failed, [ %x != %x ]", out, 3 );
        $finish;
    end
endmodule
```



Greatest Common Divisor

```
module gcd_beh #( parameter W = 16 ) (  
    input [W-1:0] inA, inB,  
    output [W-1:0] out);  
  
    reg [W-1:0] A, B, out, swap;  
    integer done;  
  
    always @(*)  
    begin  
        done = 0;  
        A = inA;  
        B = inB;  
        while (!done)  
        begin  
            if ( A < B )  
            begin  
                swap = A;  
                A = B;  
                B = swap;  
            end  
            else if ( B!=0 )  
                A=A-B;  
            else  
                done = 1;  
            end  
            out = A;  
        end  
    end  
endmodule
```

What's wrong with this approach?

Doesn't synthesize! (notice that data dependent loop?)



Making the code synthesizable

- Start with behavioral and find out what hardware constructs you'll need
 - Registers (for state)
 - Functional units
 - Adders / Subtractors
 - Comparators
 - ALU's



Identify the Hardware Structures

```
module gcd_beh #( parameter W = 16 ) (  
    input [W-1:0] inA, inB,  
    output [W-1:0] out);  
  
    reg [W-1:0] A, B, out, swap;  
    integer done;  
  
    always @(*)  
    begin  
        done = 0;  
        A ← inA;  
        B ← inB;  
        while (!done)  
        begin  
            if ( A < B )  
            begin  
                swap = A;  
                A = B;  
                B = swap;  
            end  
            else if ( B != 0 )  
                A = A - B;  
            else  
                done = 1;  
            end  
        end  
        out = A;  
    end  
endmodule
```


State → Registers

Less than comparator

Equality comparator


Subtractor

Next step: Define module ports

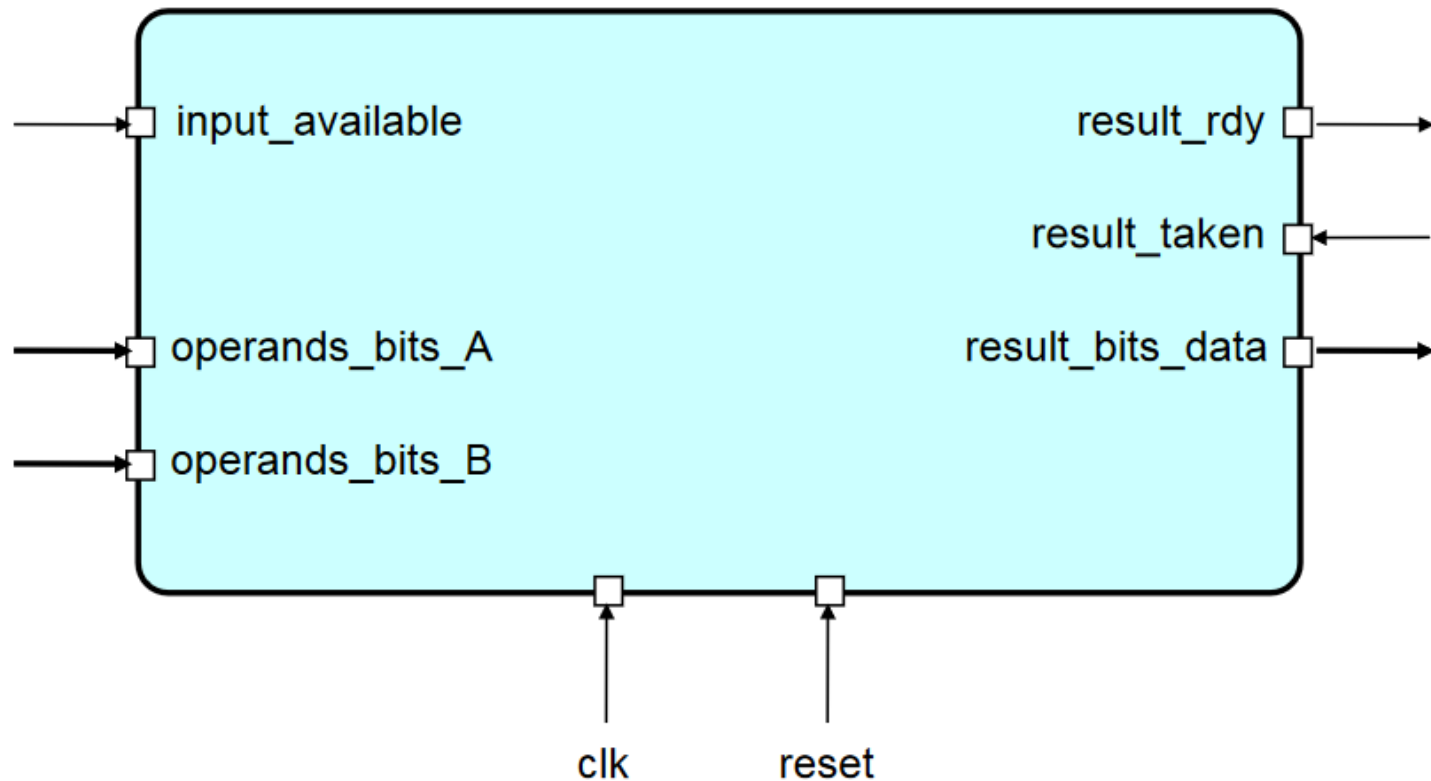


Implementing the modules

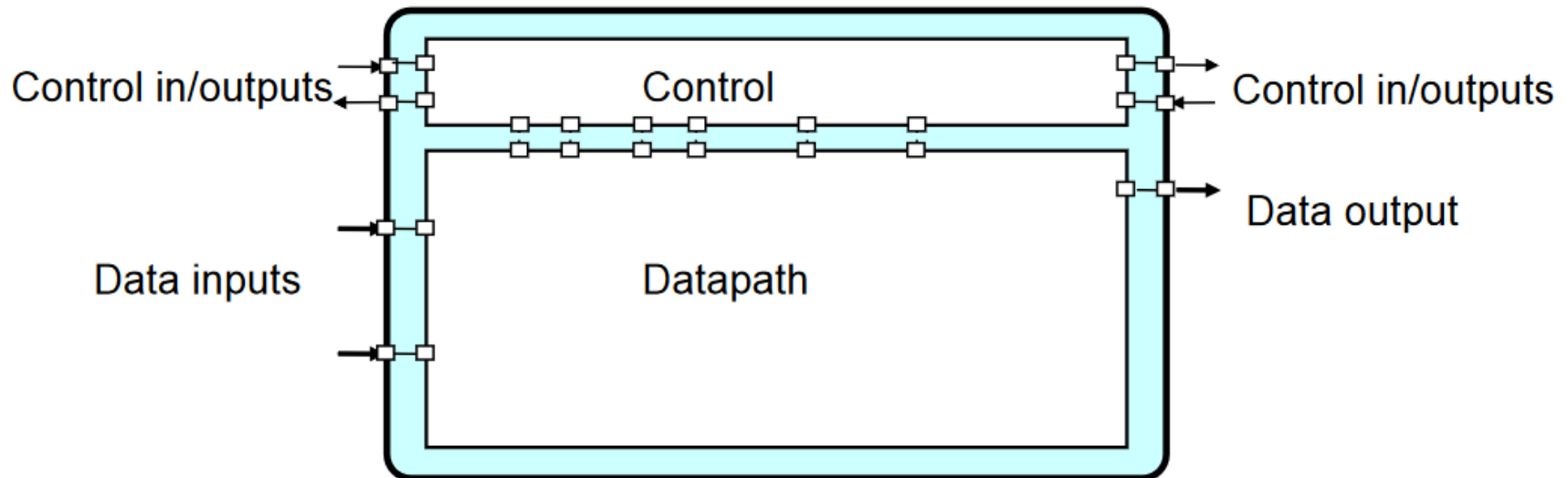
- Two step process:
 - Define datapath
 - Define controlpath




Developing the Datapath

 

Developing the Datapath

 

Developing the Datapath

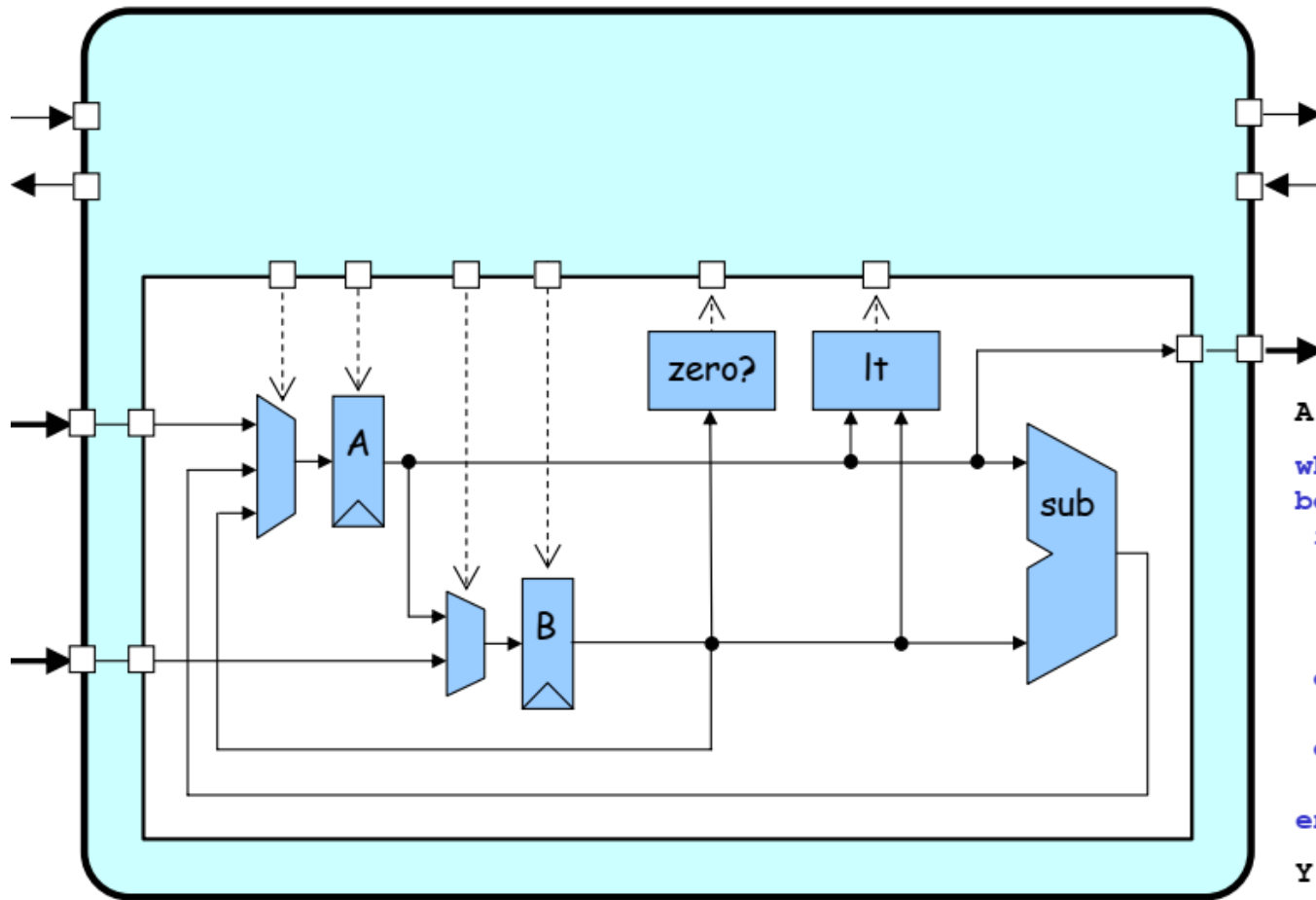


```

A = inA; B = inB;
while ( !done )
begin
  if ( A < B )
    swap = A;
    A = B;
    B = swap;
  else if ( B != 0 )
    A = A - B;
  else
    done = 1;
end
Y = A;

```


Adding Control

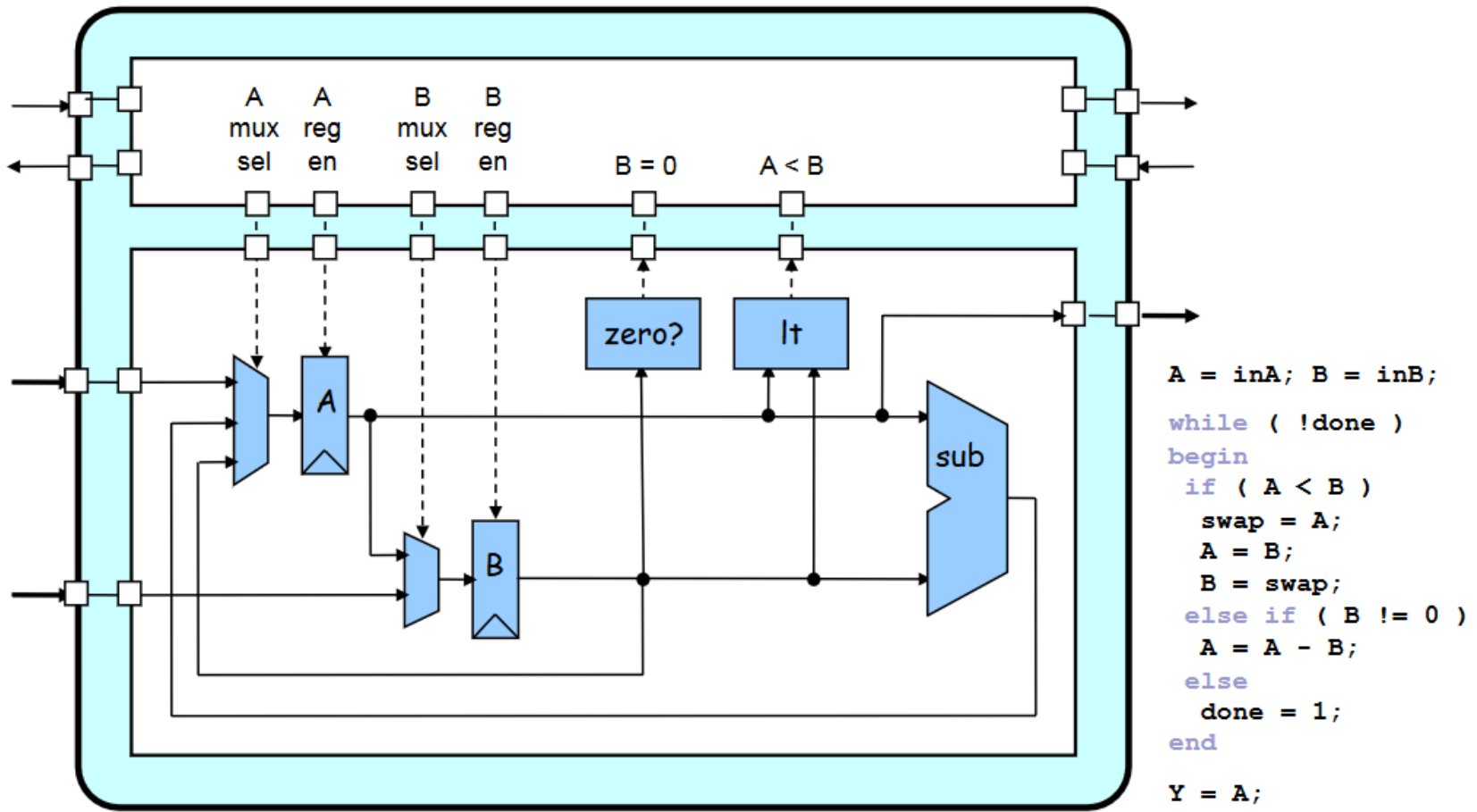

Datapath Module

```

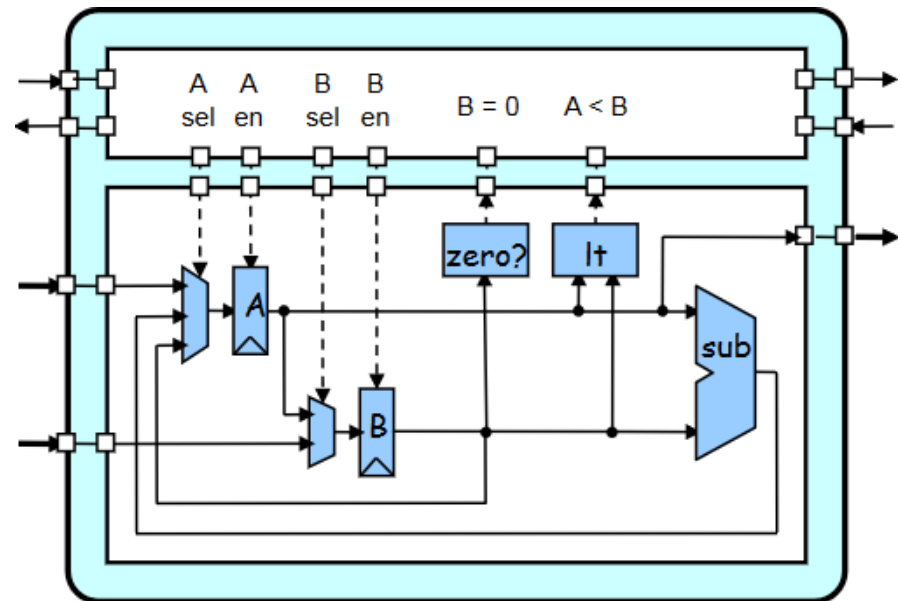module gcdDatapath#( parameter W = 16 )
(
  input      clk,
  // Data signals
  input  [W-1:0] operands_bits_A,
  input  [W-1:0] operands_bits_B,
  output [W-1:0] result_bits_data,
  // Control signals (ctrl->dpath)
  input      A_en,
  input      B_en,
  input  [1:0] A_mux_sel,
  input      B_mux_sel,
  // Control signals (dpath->ctrl)
  output      B_zero,
  output      A_lt_B
);
  
```





Implementing Datapath Module

```
wire [W-1:0] B;
wire [W-1:0] sub_out;
wire [W-1:0] A_mux_out;
3inMUX#(W) A_mux
(  .in0 (operands_bits_A),
  .in1 (B),
  .in2 (sub_out),
  .sel (A_mux_sel),
  .out (A_mux_out) );

wire [W-1:0] A;

ED_FF#(W) A_ff // D flip flop
(
    // with enable
    .clk (clk),
    .en_p (A_en),
    .d_p (A_mux_out),
    .q_np (A) );

wire [W-1:0] B_mux_out;
2inMUX#(W) B_mux (
    .in0 (operands_bits_B),
    .in1 (A),
    .sel (B_mux_sel),
    .out (B_mux_out) );

ED_FF#(W) B_ff (
    .clk (clk),
    .en_p (B_en),
    .d_p (B_mux_out),
    .q_np (B) );

2inEQ#(W) B_EQ_0 (
    .in0(B),
    .in1(W'd0),
    .out(B_zero) );

LessThan#(W) lt (
    .in0(A),
    .in0(B),
    .out(A_lt_B) );


Subtractor#(W) sub (
    .in0(A),
    .in1(B),
    .out(sub_out) );

assign result_bits_data = A;
```

Remember:
Functionality only
in “leaf” modules!



State Machine for Control

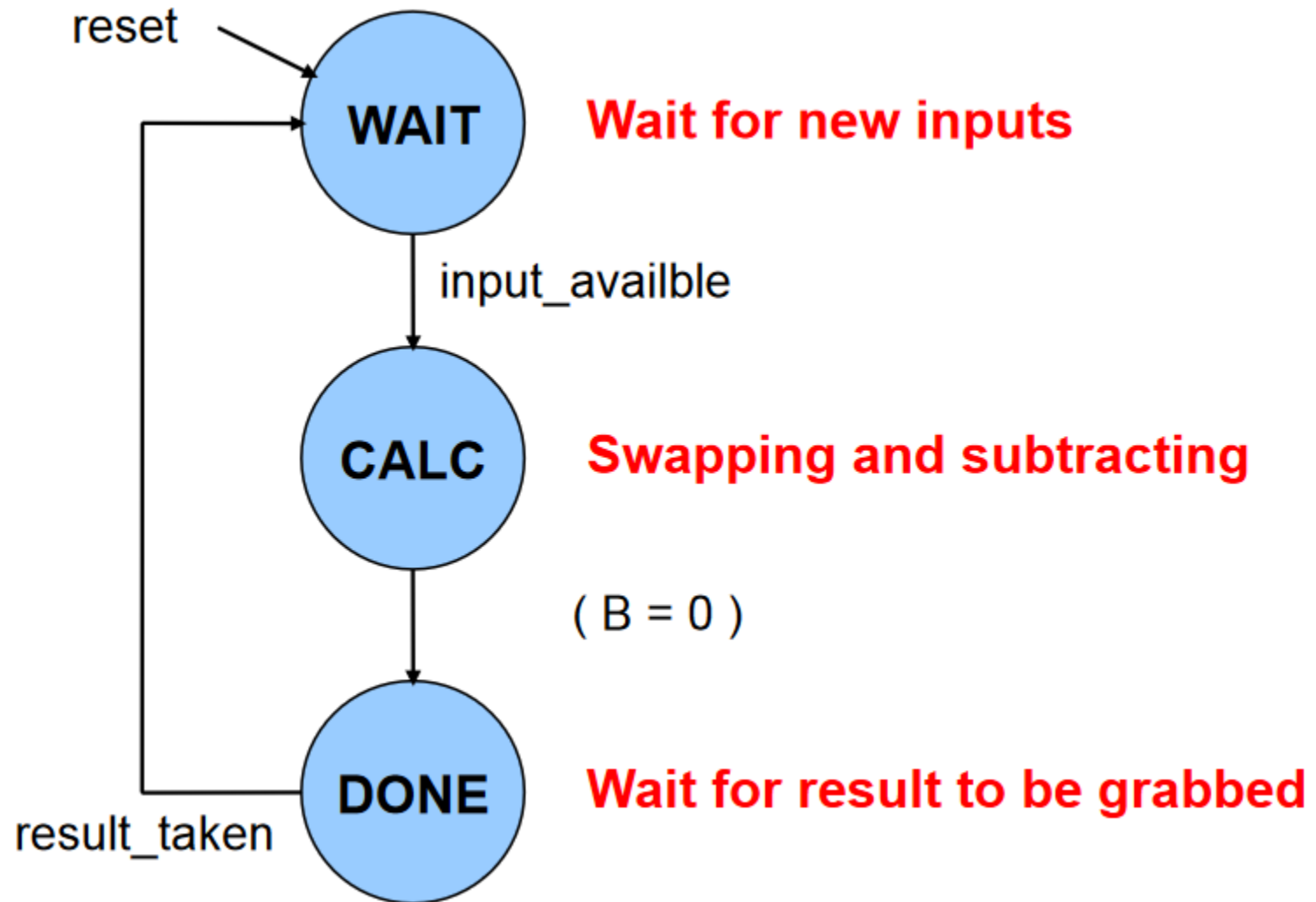

Implementing control module


```

module gcdControlUnit (
    input      clk,
    input      reset,

    // Data signals
    input      input_available,
    output reg result_rdy,
    input      result_taken,

    // Control signals (ctrl->dpath)
    output reg      A_en,
    output reg      B_en,
    output reg [1:0] A_mux_sel,
    output reg      B_mux_sel,

     // Control signals (dpath->ctrl)
    input      B_zero,
    input      A_lt_B
);
  
```





State Update Logic

- Remember: keep state update, next state calculation, and output logic separated

```
// local params are scoped constants
localparam WAIT = 2'd0;
localparam CALC = 2'd1;
localparam DONE = 2'd2;

reg [1:0] state_next;
wire [1:0] state;

RD_FF state_ff ( // flip flop with reset
    .clk (clk),
    .reset_p (reset),
    .d_p (state_next),
    .q_np (state) );
```


Output Signal Logic

```

always@(*)
begin // Default control signals
    A_mux_sel    = A_MUX_SEL_X;
    A_en         = 1'b0;
    B_mux_sel    = B_MUX_SEL_X;
    B_en         = 1'b0;

    result_rdy   = 1'b0;
    case ( state )
        WAIT :
            ...
        CALC :
            ...
        DONE :
            ...
    endcase
end

```

```

WAIT :
begin
    A_mux_sel    = A_MUX_SEL_IN;
    A_en         = 1'b1;
    B_mux_sel    = B_MUX_SEL_IN;
    B_en         = 1'b1;

end
CALC :
if ( A_lt_B )
begin
    A_mux_sel    = A_MUX_SEL_B;
    A_en         = 1'b1;
    B_mux_sel    = B_MUX_SEL_A;
    B_en         = 1'b1;

end
else if ( !B_zero )
begin
    A_mux_sel    = A_MUX_SEL_SUB;
    A_en         = 1'b1;


end

DONE :
    result_rdy = 1'b1;


```

Next State Logic
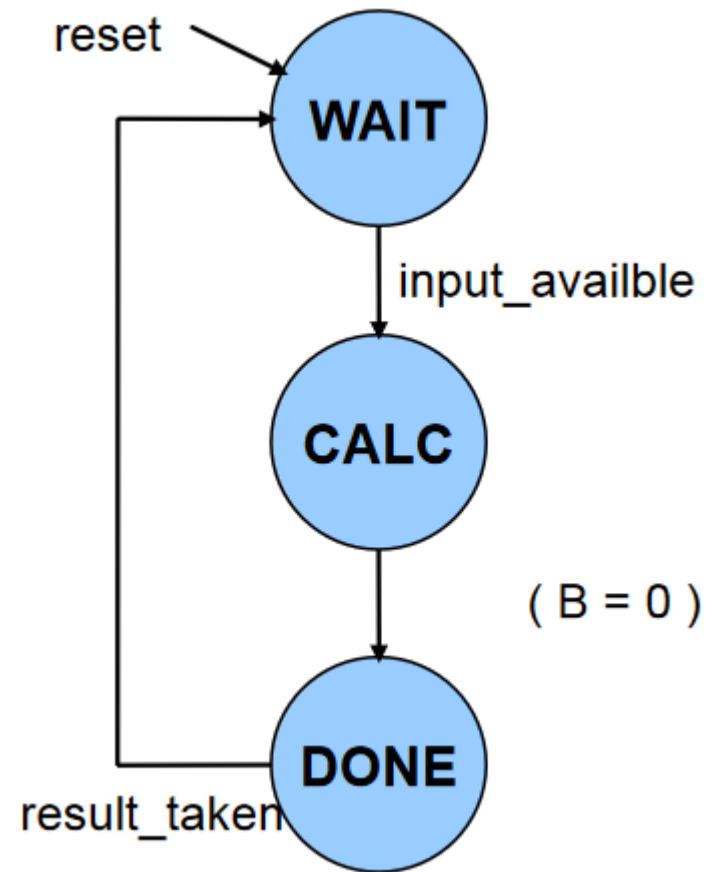
```
always @(*)
begin
    // Default is to stay in
    // the same state
    state_next = state;
    case ( state )
        WAIT :
            if ( input_available )
                state_next = CALC;
        CALC : if ( B_zero )
                state_next = DONE;
        DONE : if ( result_taken )
                state_next = WAIT;
    endcase
end
```



Next Step: Define Module Ports

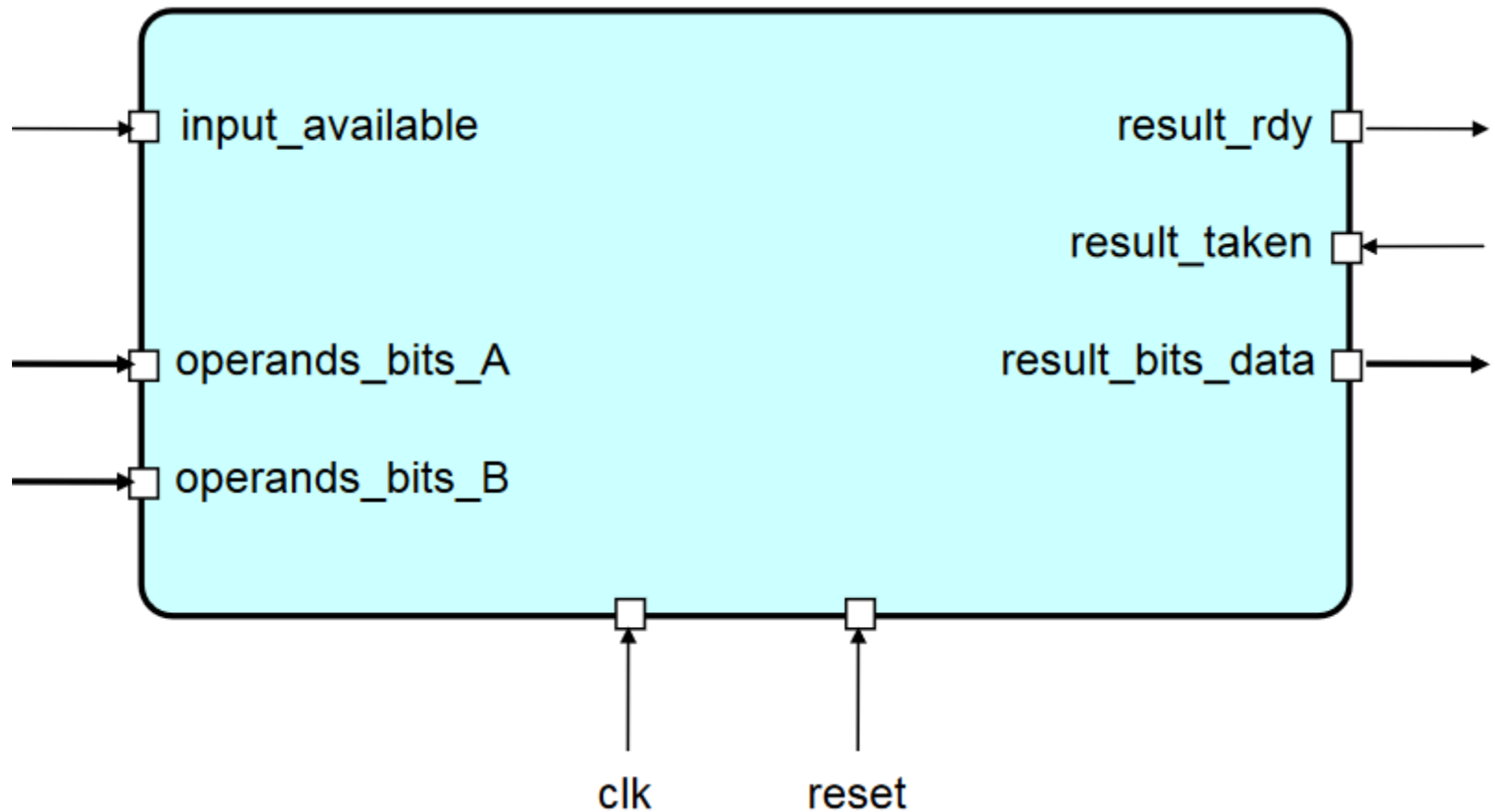

Wire them together

```


module gcd#( parameter W = 16 )
(
    input      clk,
    // Data signals
    input  [W-1:0] operands_bits_A,
    input  [W-1:0] operands_bits_B,
    output [W-1:0] result_bits_data,
    // Control signals
    input input_available,
    input reset,
    output result_rdy,
    input result_taken
);

```

```

wire[1:0] A_sel;
wire A_en;
...
...

```

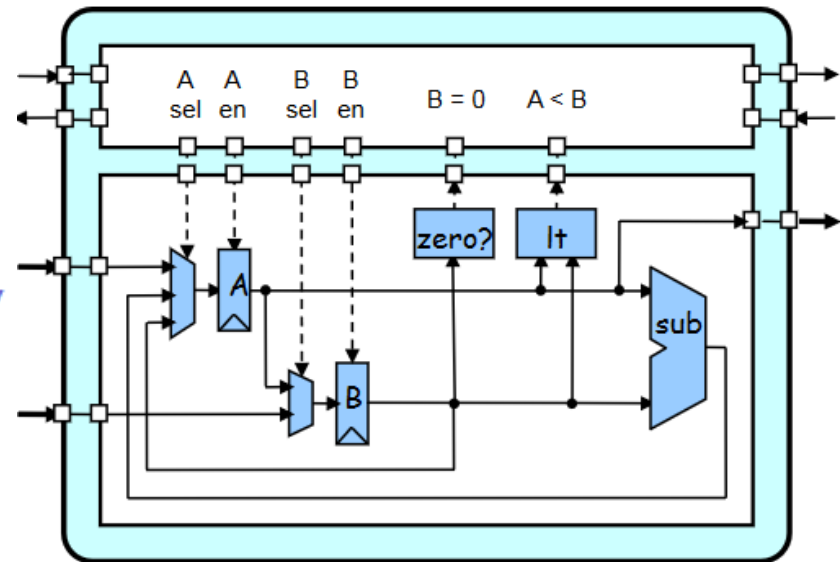

```

gcdDatapath#(16) datapath (
    .operand_bits_A(operands_bits_A),
    ...
    .A_mux_sel(A_sel),
    ...
)
gcdControl#(16) control (
    .A_sel(A_sel),
    ...
)

```



References

- Mentioned in the first slide 😊

Thank you