


Digital Design with Verilog

Lecture 2: Review of Combinational Logic Design



Combinational Logic

 - Combinational logic forms its outputs as Boolean functions of its input variables on an instantaneous basis.



Block diagram symbol for combinational logic

- At any time t the outputs y_1 , y_2 , and y_3 depend on only the values of a , b , c , and d at time t .

Common Logic Gates


AND Gate

$$y = a \cdot b$$




OR Gate

$$y = a + b$$

 

XOR Gate

$$y = a \wedge b$$

 


NAND Gate

$$y = \overline{a \cdot b}$$




NOR Gate

$$y = \overline{a + b}$$

 


XNOR Gate

$$y = \overline{a \wedge b}$$

 


Buffer

$$y = a$$

 


Inverter

$$y = \overline{a}$$

 

Three-State Buffer
 
$$y = a \text{ if enable} = 1, \text{ else } y = z$$




Schematic symbols and Boolean relationships for some common logic gates.



Boolean Logic Symbols and Operations


Symbol	Logic Operation
$+$	Logic “or”
\cdot	Logical “and”
\oplus	Exclusive “or”
\wedge	Exclusive “or”
$'$	Logical negation
$-$	Logical negation (overbar)

ASIC Library Cells

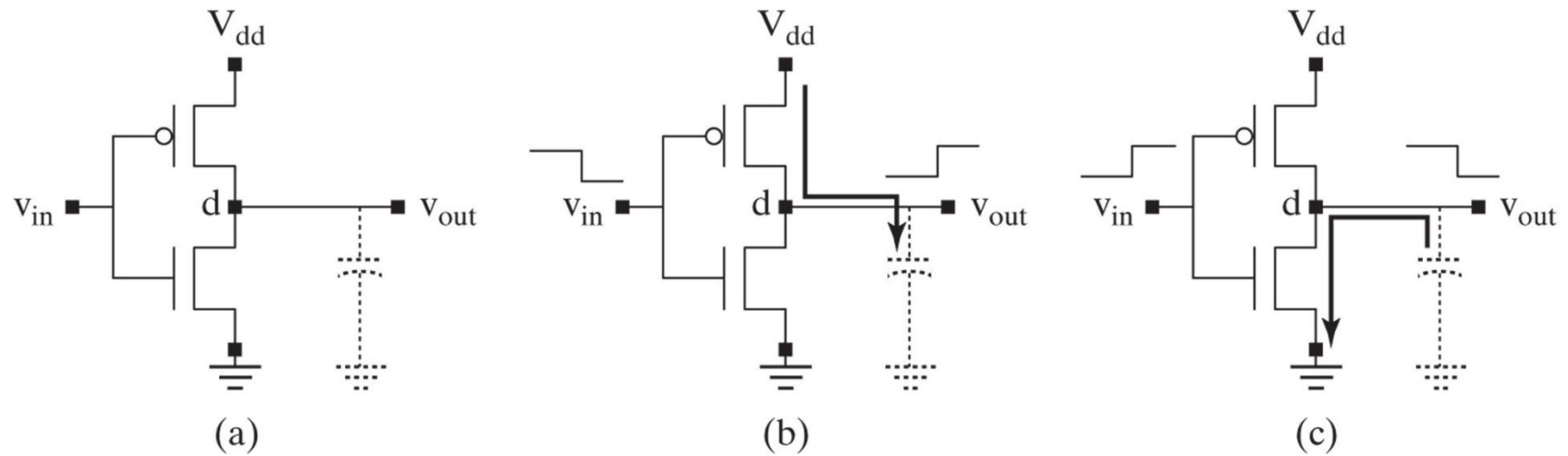


CMOS transistor-level schematics: (a) inverter with output load capacitance, (b) inverter with pull-up (charging) signal paths, and (c) inverter with pull-down (discharging) signal paths.

Three input CMOS NAND Gate

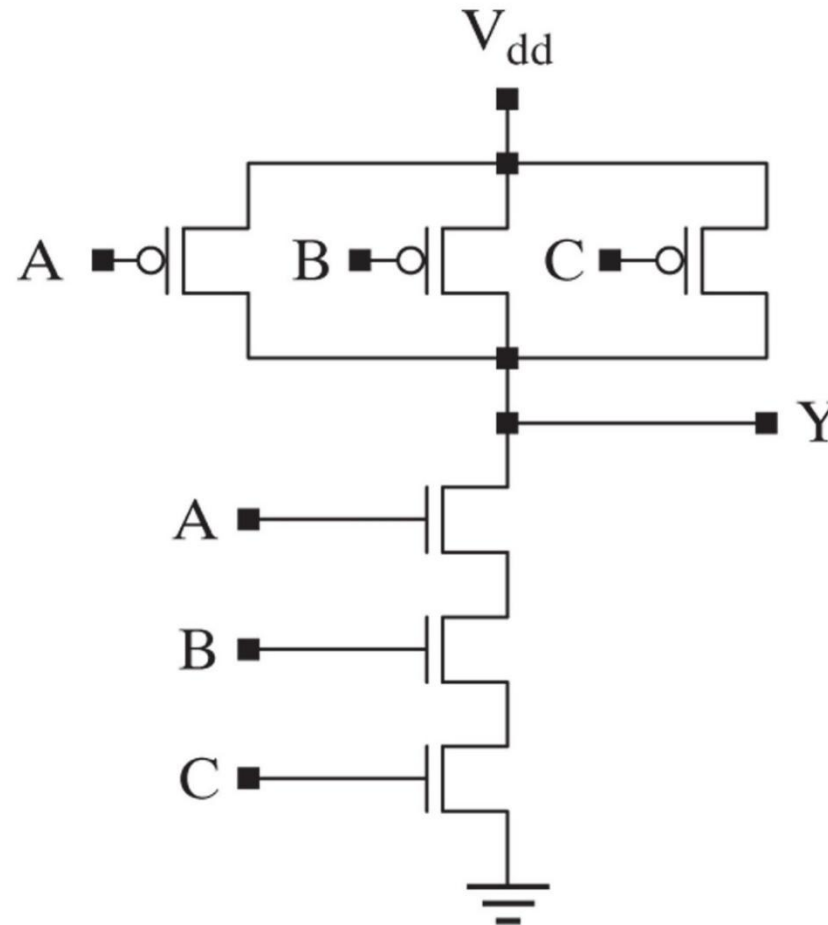


Views of a CMOS Inverter

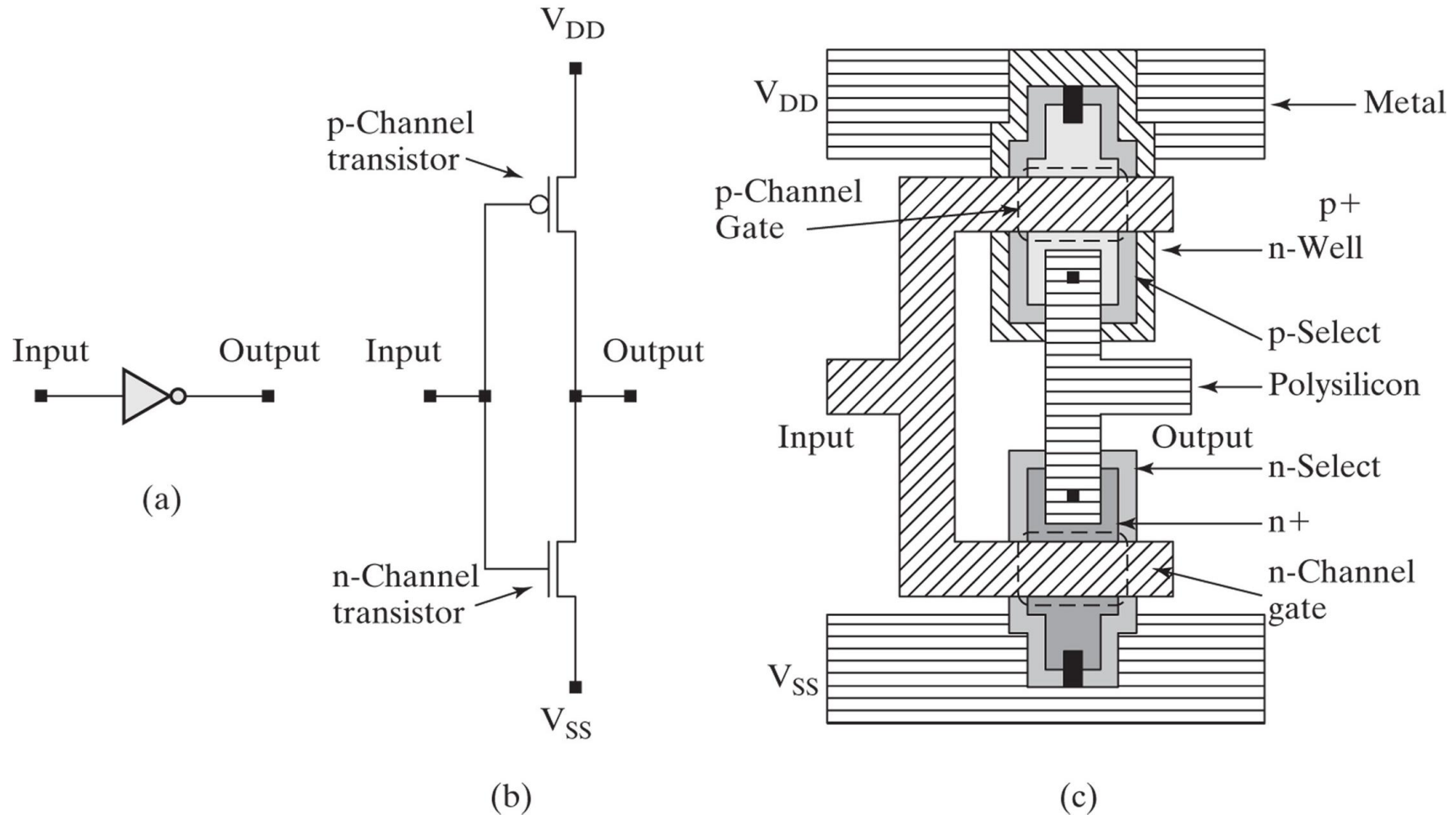

Views of a CMOS inverter: (a) circuit-symbol view, (b) transistor-schematic view, and (c) simplified composite fabrication mask view.

Inverter-Cross Section

 

Simplified side view showing the doping regions of a CMOS inverter.

Standard Cell Library


- Circuits that implement basic and moderately complex Boolean functions are characterized for
 - Functional, electrical, and timing properties,
 - Packaged in a library for repeated use in multiple designs.
- Such libraries commonly contain basic logic gates, flip-flops, latches, muxes, and adders.
- Synthesis tools build complex integrated circuits by mapping the result of logic synthesis onto the parts of a cell library to implement the specified functionality with acceptable performance.

Boolean Algebra

- The operations of logic circuits are described by Boolean algebra.
- A Boolean algebra consists of a set of values $B = \{0, 1\}$ and the operators "+" and "·".

Laws of Boolean Algebra	SOP Form	POS Form
Combinations with 0, 1	$a + 0 = a$	$a \cdot 1 = a$
	$a + 1 = 1$	$a \cdot 0 = 0$
Commutative	$a + b = b + a$	$ab = ba$
Associative	$(a + b) + c = a + (b + c)$ $= a + b + c$	$(ab)c = a(bc) = abc$
Distributive	$a(b + c) = ab + ac$	$a + bc = (a + b)(a + c)$
Idempote	$a + a = a$	$a \cdot a = a$
Involution	$(a')' = a$	
Complementarity	$a + a' = 1$	$a \cdot a' = 0$


Boolean Space

 

Points in a Boolean space: (a) represented by vectors of binary variables and (b) represented symbolically.


DeMorgan's Laws

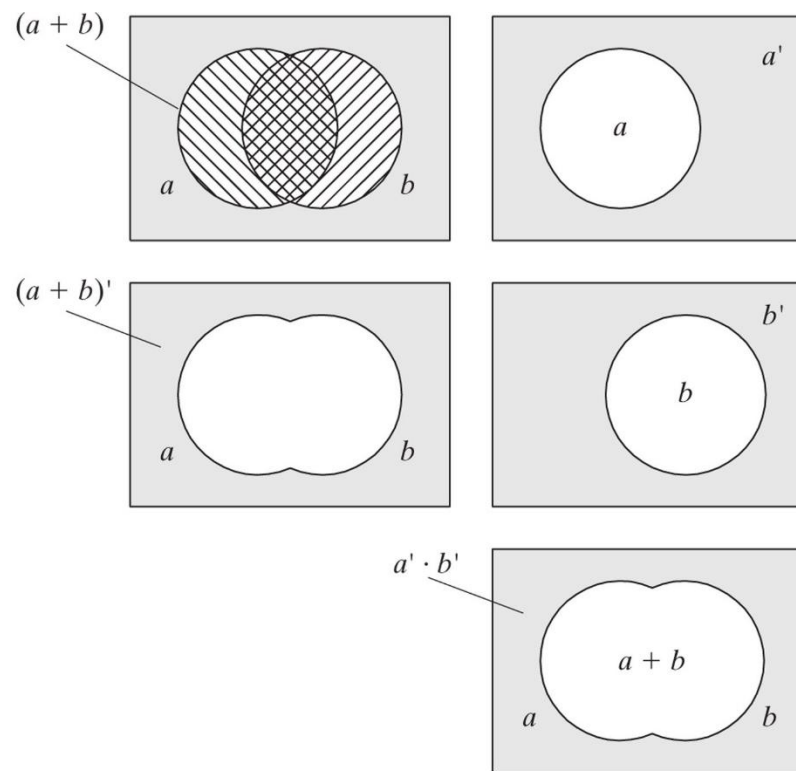- DeMorgan's laws allow us to transform a circuit from an SOP form to a POS form, and vice versa.



Venn diagrams illustrating DeMorgan's law: $(a + b)' = a' \cdot b'$

DeMorgan's Laws

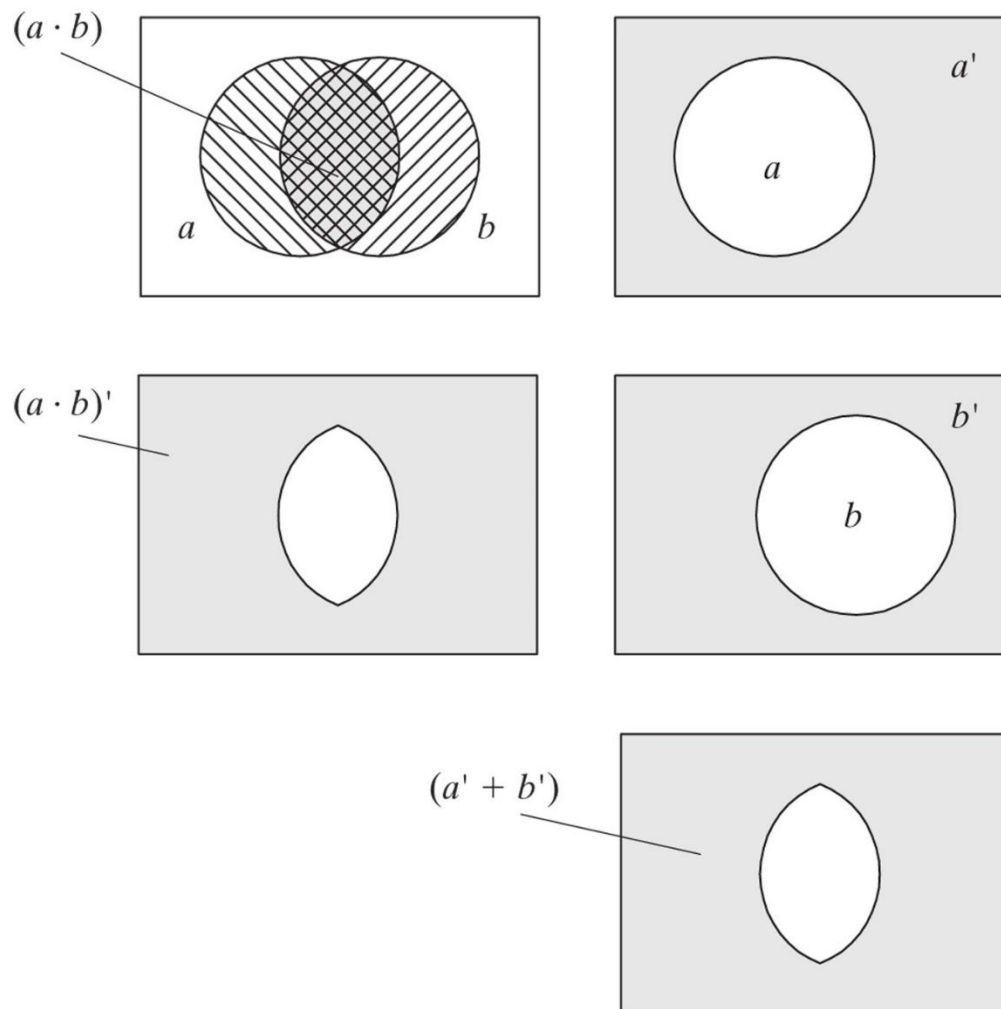


Venn diagrams illustrating DeMorgan's law: $(a \cdot b)' = a' + b'$.

Theorems for Boolean Algebraic Minimization

Theorem	SOP form	POS form
Logical adjacency	$ab + ab' = a$	$(a + b)(a + b') = a$
Absorption or	$a + ab = a$ $ab' + b = a + b$ $a + a'b = a + b$	$a(a + b) = a$ $(a + b')b = ab$ $(a' + b)a = ab$
Multiplication and factoring	$(a + b)(a' + c) = ac + a'b$	$ab + a'c = (a + c)(a' + b)$
Consensus	$ab + bc + a'c = ab + a'c$	$(a + b)(b + c)(a' + c) =$ $(a + b)(a' + c)$

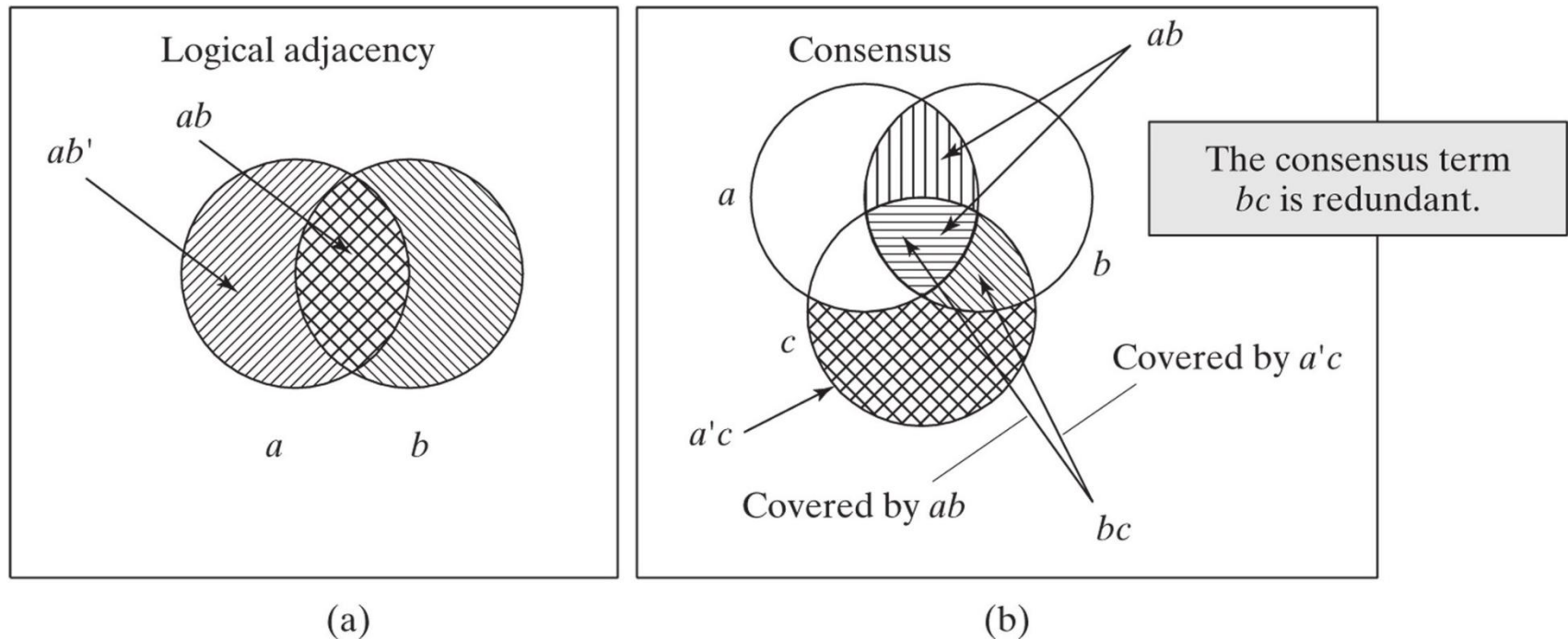Theorems for Boolean Algebraic Minimization



Venn diagrams: (a) logical adjacency and (b) consensus.

Exclusive-OR laws

Exclusive-OR laws	
Combinations with 0, 1	$a \oplus 0 = a$ $a \oplus 1 = a'$ $a \oplus a = 0$ $a \oplus a' = 1$
Commutative	$a \oplus b = b \oplus a$
Associative	$(a \oplus b) \oplus c = a \oplus (b \oplus c) = a \oplus b \oplus c$
Distributive	$a(b \oplus c) = ab \oplus ac$
Complement	$(a \oplus b)' = a \oplus b' = a' \oplus b = ab + a'b'$


Representation of Combinational Logic

- Three common representations of combinational logic:
 - Structural (i.e., gate-level) schematics
 - Truth tables
 - Boolean equations
- Binary decision diagram (BDD)s are used primarily within EDA software tools because they can be more efficient and easier to manipulate than truth tables.


Half Adder

Inputs		Outputs	
<i>a</i>	<i>b</i>	<i>c_out</i>	<i>sum</i>
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

(a)

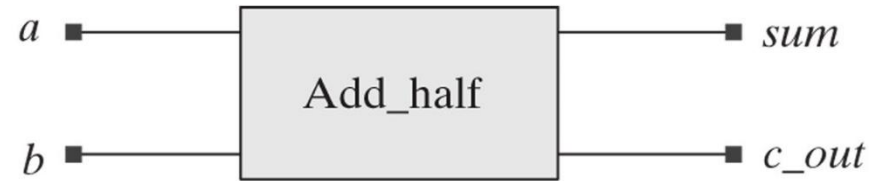

(b)

 


(c)

Half adder: (a) truth table, (b) block diagram symbol, and (c) schematic.


Full Adder

Inputs			Outputs	
a	b	c_{in}	c_{out}	sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

(a)

 

(b)

 

(c)

Full adder: (a) truth table, (b) block diagram symbol, and (c) schematic for a full adder composed of half adders and glue logic.

Sum-of-Products Representation


- A cube is formed as the product of literals in which a literal appears in either uncomplemented or complemented form.
- A *Boolean expression* is a set of cubes and is typically expressed in an SOP form as the "OR" of product terms (cubes), rather than in set notation.
- A *minterm* is a cube in which every variable appears. The variable will be in either true (uncomplemented) or complemented form (but not both).



Sum-of-Products Representation

- A Boolean expression in SOP form is said to be **canonical** if every cube in the expression has a unique representation in which all of the literals are in complemented or uncomplemented form.
- A **canonic** (standard) SOP function is also called a standard sum of products (SSOP).
- A **Boolean function** is a set of minterms (vertices) at which the function is asserted. A Boolean function in SOP form is expressed as a sum of minterms.

Sum-of-Products Representation

 

Correspondence between minterms and vertices in \mathbf{B}^3 .

$$\begin{aligned} \text{sum} &= m_1 + m_2 + m_4 + m_7 = \Sigma m(1, 2, 4, 7) \\ \text{c_out} &= m_3 + m_5 + m_6 + m_7 = \Sigma m(3, 5, 6, 7) \end{aligned}$$

Products-of-Sums Representation

- A Boolean function can also be expressed in a POS form in which the expression is written as a product of Boolean factors, each of which is a sum of literals.
- A Boolean expression in POS form is said to be *canonical* (i.e., a unique representation for a given function) if each factor has all of the literals in complemented or uncomplemented form, but not both.
- A *maxterm* is an OR-ed sum of literals in which each variable appears exactly once in true or complemented form.

Simplification of Boolean Functions

- Minimization is important because the cost of hardware implementing a Boolean expression is related to
 - The number of terms in the expression and
 - The the number of literals in a term, that is, in a cube in an SOP expression.
- A Boolean expression in SOP form is said to be *minimal*, if it contains a minimal number of product terms and literals (i.e., a given term cannot be replaced by another that has fewer literals).



Simplification of Boolean Functions

- Approaches for minimizing Boolean Expressions:

Application of Boolean theorems,

Karnaugh maps,

Quine-McCluskey minimization, and


Synthesis tools (Espresso-II).

Simplification of Boolean Functions

- Logic minimization searches for efficient representations of Boolean functions.
- In a Boolean expression, a cube that is contained in another cube is said to be redundant---a cube is *redundant* if its set of vertices is properly contained in the set of vertices of another cube of the function.
- A Boolean expression is *nonredundant (irredundant)* if no cube contains another cube.
- The cubes of an irredundant expression do not share a common vertex, that is, their corresponding sets of vertices are pairwise disjoint


Building Blocks for Logic Design

NAND-NOR Structures

 

Circuit transformations to obtain a NAND/Inverter realization of an SOP expression.


NAND-NOR Structures

 

Circuit transformations to obtain a NOR/Inverter realization of a POS expression.

Multiplexers

 
- Multiplexer circuits are used to steer data through functional units of computers and other digital systems.




Gate-level schematic for a two-channel multiplexer circuit.

Multiplexers/Data selectors

 - A **multiplexer** is a combinational circuit that selects binary information from one of many input lines and directs it to a single output line.
 - The selection of a particular input line is controlled by a set of selection lines.
 - Normally, there are 2^n input lines and n selection lines whose bit combinations determine which input is selected.




(a) Logic diagram

 

(b) Block diagram

4x1 multiplexer

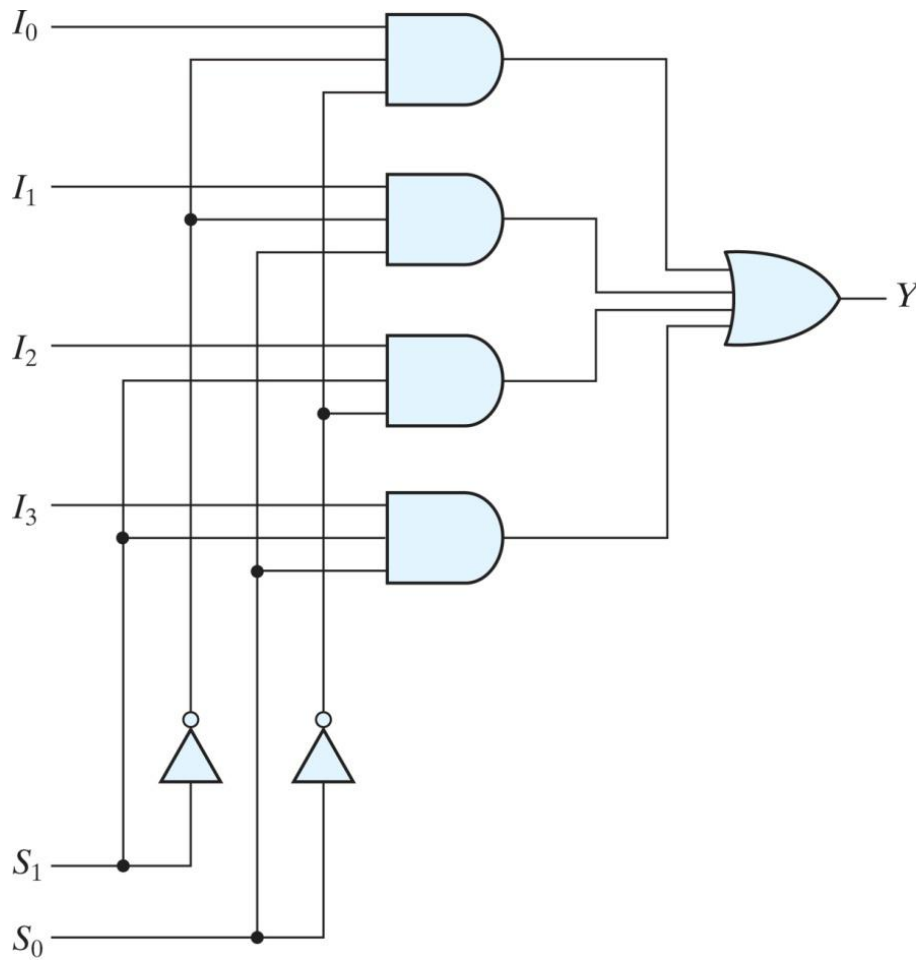



(a) Logic diagram

S_1	S_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

  (b) Function table


Demultiplexer

- Multiplexer (MUX)
 - Routes one of many inputs to a single output
 - Also called a *selector*
- Demultiplexer (DEMUX)
 - Single data input; n control inputs (“selects”); 2^n outputs
 - Single input connects to one of 2^n outputs
 - “Selects” decide which output is connected to the input



3x8 Demux

 - The input is called an “enable” (**G**)



3:8 Decoder:

$$\begin{aligned} \text{Out0} &= G \bullet S2' \bullet S1' \bullet S0' \\ \text{Out1} &= G \bullet S2' \bullet S1' \bullet S0 \\ \text{Out2} &= G \bullet S2' \bullet S1 \bullet S0' \\ \text{Out3} &= G \bullet S2' \bullet S1 \bullet S0 \\ \text{Out4} &= G \bullet S2 \bullet S1' \bullet S0' \\ \text{Out5} &= G \bullet S2 \bullet S1' \bullet S0 \\ \text{Out6} &= G \bullet S2 \bullet S1 \bullet S0' \\ \text{Out7} &= G \bullet S2 \bullet S1 \bullet S0 \end{aligned}$$

Encoders

- An encoder is a digital circuit that performs the inverse operation of a decoder. An encoder has 2^n (or fewer) input lines and n output lines.

Truth Table of an Octal-to-Binary Encoder

Inputs								Outputs		
D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7	x	y	z
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

- It is assumed that only one input has a value of 1 at any given point in time.

Encoders (Contd.)

- The encoder can be implemented with OR gates whose inputs are determined directly from the truth table.

$$z = D_1 + D_3 + D_5 + D_7$$

$$y = D_2 + D_3 + D_6 + D_7$$

$$x = D_4 + D_5 + D_6 + D_7$$

- Two problems
 - What if two inputs are active simultaneously?
 - Output with all 0's generated when all the inputs are 0; but this same as when D_0 is equal to 1.

Priority Encoder

- A **priority encoder** is an encoder circuit that includes the priority function. The operation of the priority encoder is such that if two or more inputs are equal to 1 at the same time, the input having the highest priority will take precedence.

Truth Table of a Priority Encoder

Inputs				Outputs		
D_0	D_1	D_2	D_3	x	y	V
0	0	0	0	X	X	0
1	0	0	0	0	0	1
X	1	0	0	0	1	1
X	X	1	0	1	0	1
X	X	X	1	1	1	1

- Input D_3 has the highest priority.

Decoders

- A decoder is a combinational circuit that converts binary information from n input lines to an 2^n unique output lines.
- Some Applications:
 - Microprocessor memory system: selecting different banks of memory.
 - Microprocessor I/O: Selecting different devices.
 - Memory: Decoding memory addresses (e.g. in ROM).

2-to-4-line DECODER with Enable

- The decoder is enabled when $E = 0$. The output whose value = 0 represents the minterm is selected by inputs A and B .
- The decoder is inactive when $E = 1 \rightarrow D_0 \dots D_3 = 1$
 - A Decoder with enable input is called a decoder/demultiplexer.
- Demultiplexer receives directs it to the output I

E	A	B	D_0	D_1	D_2	D_3
1	X	X	1	1	1	1
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0

Thank you