

Digital Design with Verilog

Verilog - Synthesis

Lecture 19: Logic Synthesis with Verilog HDL – Part2





Objectives

- Synthesis of Verilog Constructs
 - Logical Operators
 - Arithmetic Operators
 - Shift operators
 - Case operators
 - Vector Operators -Part Select


Logical Operators

- Logical Operators get directly mapped onto primitive logic gates in hardware.

```
module FullAdder (A, B, Carryin, Sum, CarryOut);  
    input A, B, Carryin;  
    output Sum, CarryOut;  
  
    assign Sum = (A ^ B) ^ Carryin;  
    assign CarryOut = (A & B) | (B & Carryin) | (A & Carryin);  
endmodule
```

- This gets modeled as 3, 2-input AND; 2, 2-input OR and 2, 2-input XOR.

Synthesized Circuit

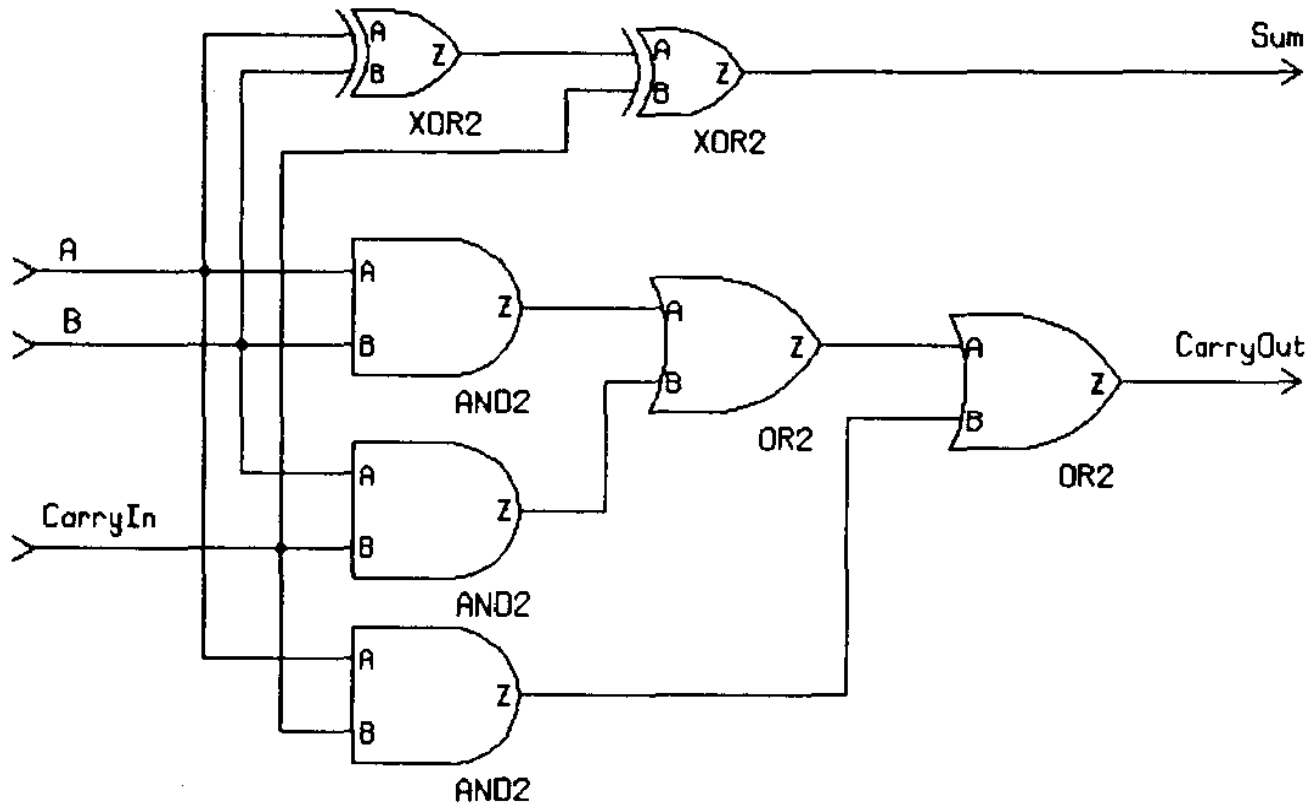

Logical operators map to primitive logic gates.


Arithmetic Operators

- A **reg** type is interpreted as an unsigned number and an **integer** type is interpreted as a signed number in 2's complement form with the rightmost bit as the least significant bit.
- Thus, to synthesize an unsigned arithmetic operator, the **reg** type is used.
- To get a signed arithmetic operator, the **integer** type is used.
- The **net** type is interpreted as unsigned numbers.

Unsigned Arithmetic

```
module UnsignedAdder (Arb, Bet, Lot);  
    input [2:0] Arb, Bet;  
    output [2:0] Lot;  
  
    assign Lot = Arb + Bet;  
  
endmodule
```

Unsigned Arithmetic

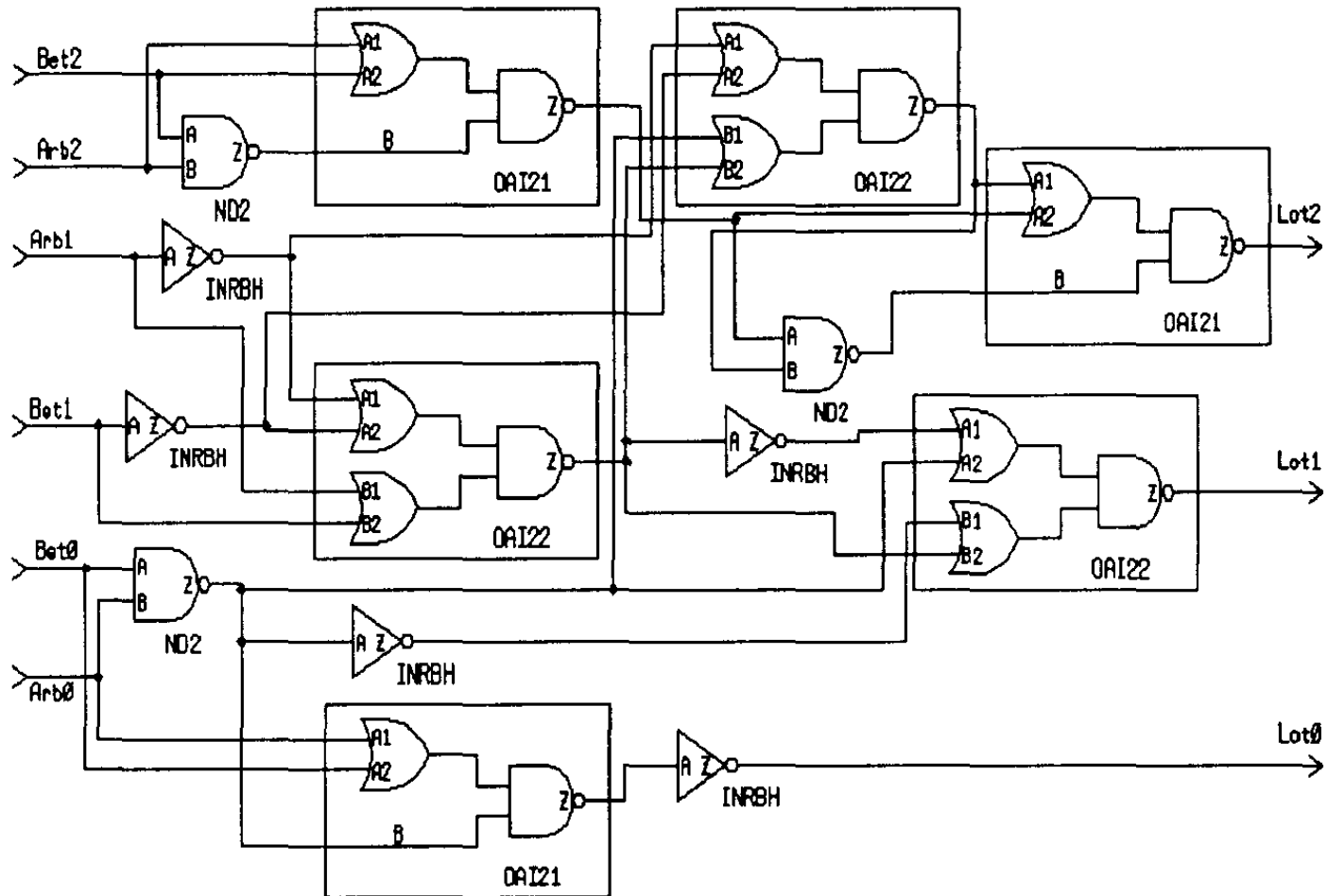


A 3-bit adder



Signed Arithmetic

```
module SignedAdder (Arb, Bet, Lot);  
    input [1:0] Arb, Bet;  
    output [2:0] Lot;  
  
    reg [2:0] Lot;  
  
    always @ (Arb or Bet)  
    begin: LABEL_A  
        //A sequential block requires a label if local  
        //declarations are present.  
  
        integer Arbint, Betint;  
  
        .... Arbint = - Arb; // Store negative number just to show  
                           //that the + is operating on signed operands.  
        Betint = Bet;  
        Lot = Arbint + Betint;  
    end  
endmodule
```


Synthesized Circuit

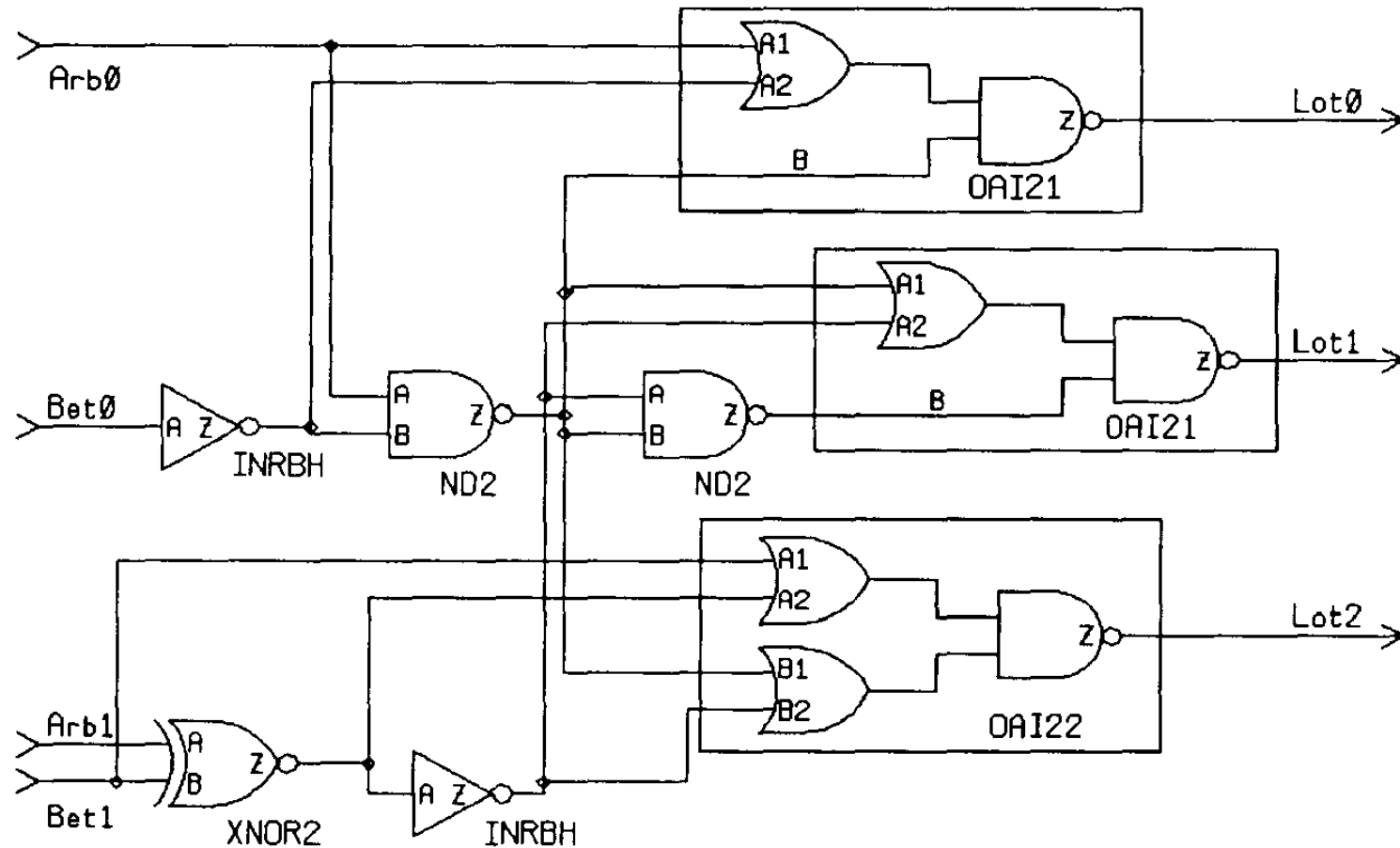

Signed adder



Synthesized Circuit

- The synthesized circuit will be a 2-bit adder and not a 32-bit one.
- How it is found –Due to ‘Lot’ or Due to “Arb” or “Bet”.
- The adder logic with signed and unsigned operands is the same, as signed numbers are stored in 2's complement form.

Modeling a Carry

- It is natural to model a carry by simply using the result size to be one bit larger than the largest of the two operands.
- Alternatively, a concatenation could also be used as the target of an assignment with the carry bit explicitly specified.

```
wire [3 :0] CdoBus, Sum;  
wire [4:0] OneUp;  
wire Bore;  
assign OneUp = CdoBus + 1;  
assign {Bore, Sum} = CdoBus - 2;
```

Relational and Equality Operators

- $>$, $<$, \leq , \geq , $==$, $!=$
- Modeled like Arithmetic operators.
- Logic produced from Synthesis is different, depending on whether unsigned or signed.
- If variables of net or reg types are compared then, unsigned relational operator is synthesized
- If variables of integer types are compared then, signed relational operator is synthesized.


Relational Operators

```

module GreaterThan (A, B, Z);
    input [3:0] A, B;
    output Z;

    assign z = A[1:0] > B[3:2];
    //Variables A and B are of net type.
endmodule

```

 


Unsigned ">" relational operator



Relational Operators

```
module LessThanEquals (ArgA, ArgB, ResultZ);  
    input [2:0] ArgA, ArgB;  
    output ResultZ;  
    reg ResultZ;  
    integer ArgAInt, ArgBInt;  
  
    always @ (ArgA or ArgB)  
    begin  
        ArgAInt = - ArgA;  
        ArgBInt = - ArgB;  
  
        //Store negative values just to show that the  
        //comparison is on signed numbers.  
        ResultZ = ArgAInt <= ArgBInt;  
    end  
endmodule
```

Relational Operators

 


Signed " \leq " relational operator.

Equality Operators

- The equality operators supported are: ==, !=

```
module NotEquals (A, B, Z);  
input [0:3] A, B;  
output Z;  
reg Z;  
    always @ (A or B)  
begin: DF_LABEL  
    integer IntA, IntB;  
    IntA =A;  
    IntB = B;  
    Z = IntA != IntB;  
end  
endmodule
```


Equality Operators

 

Signed "!=" relational operator

Case Operators

- Case equality and Case inequality operators (===) and (!==) are not supported for synthesis.

Shift Operators


- For synthesis, the left shift (\ll) and the right shift (\gg) operators are supported.
- The vacated bits are filled with 0.
- If the amount of shift is a constant then, simple rewiring is done, else a general-purpose shifter is synthesized

Shift Operators

```

module ConstantShift (DataMux, Address);
input [0:3] DataMux;
output [0:5] Address;
    assign Address = (~DataMux) << 2;
endmodule

```

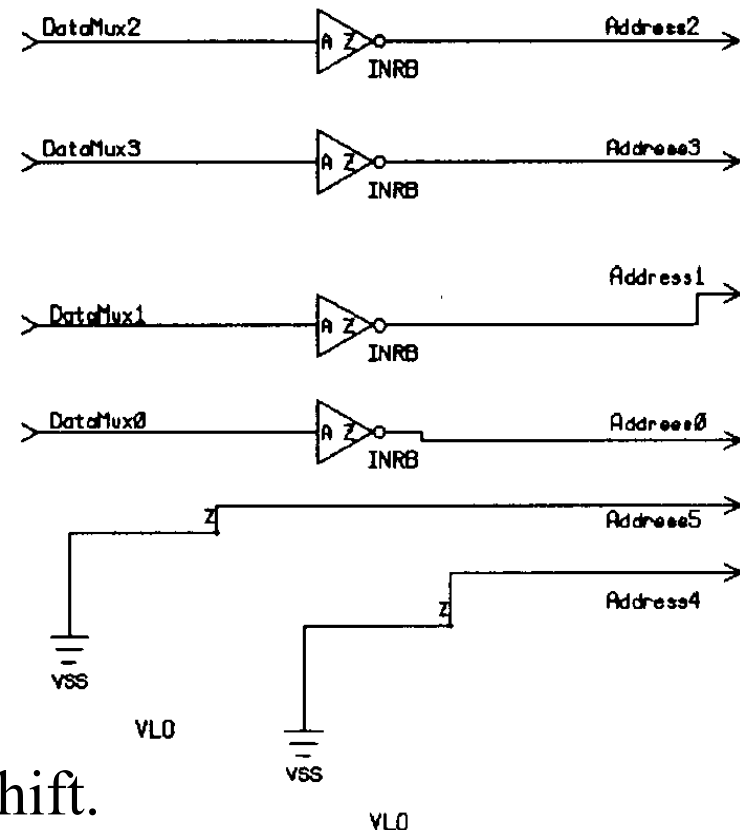


Constant shift.



Shift Operators

```
module VariableShift (MemDataReg, Amount, InstrReg);  
    input [0:2] MemDataReg;  
    input [0:1] Amount;  
    output [0:2] InstrReg;  
    assign InstrReg = MemDataReg >>Amount;  
endmodule
```

Shift Operators

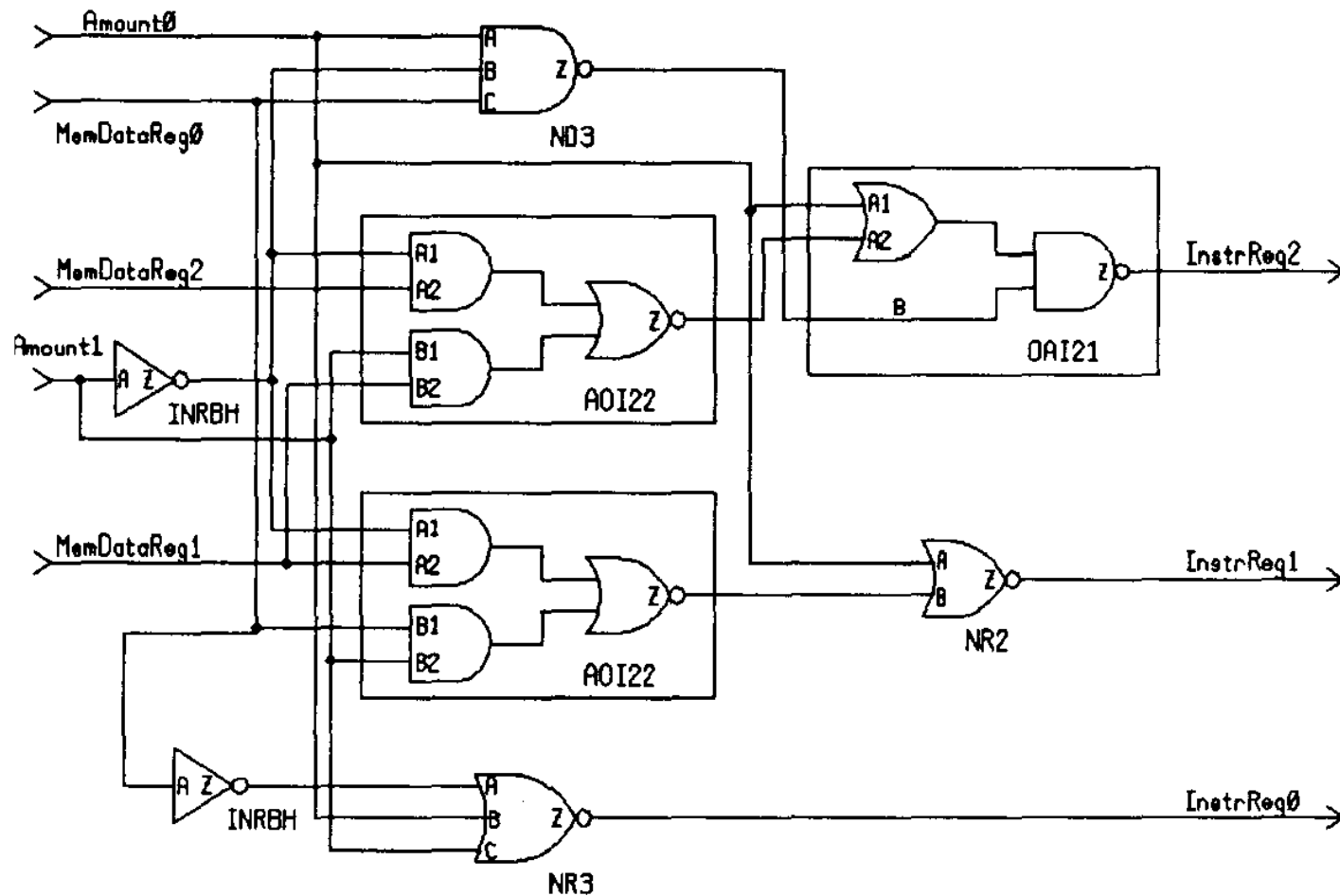


Variable shift



Vector Operations

```
module VectorOperations (A, B, C, RFile);  
    input [3:0] A, B, C;  
    output [3:0] RFile;  
  
    assign RFile = (A & B) | C;  
endmodule
```

Vector Operations

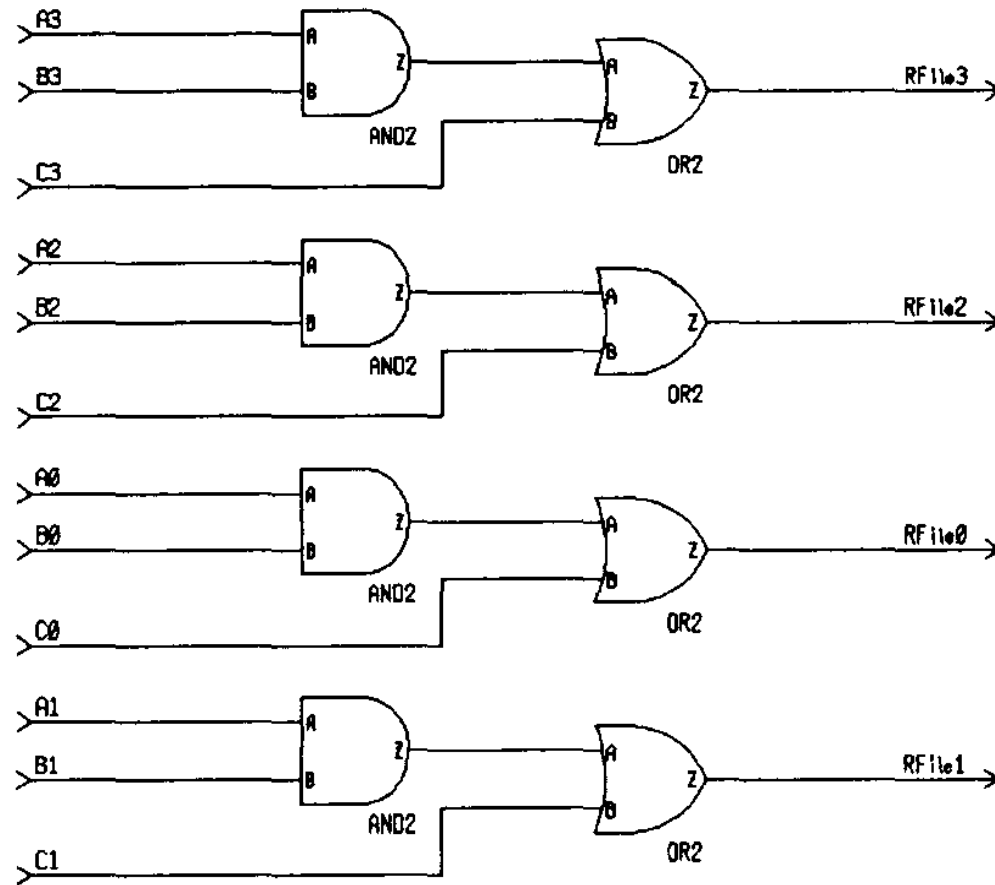





Vector operations.

Vector Operations

```

module VectorOperands (Bi, Stdy, Tap);
    input [0:3] Bi, Stdy;
    output [0:3] Tap;
    assign Tap = Bi ^ Stdy;
endmodule

```

    


A bank of logic gates

Part-selects

```
module PartSelect (A, C, ZCat) ;  
input [3:0] A, C;  
output [3:0] ZCat;  
    assign ZCat [2:0] = {A[2], C[3:2]};  
endmodule
```

- Rule: Non-constant part-selects are not supported in VerilogHDL

Part-selects

 

Part-select example.

Bit-Selects and Assignment


- A bit-select can be a constant index or a non-constant index.
 - Constant Index in Expression/Target.
 - Non-Constant Index in Expression.
 - Non-Constant Index in Target



Constant Index

```
module Constantindex (A, C, Reg_File, ZCat);  
    input [3:0] A, C;  
    input [3:0] Reg_File;  
    output [3:0] ZCat;  
  
    assign ZCat[3:1] = {A[2], C[3:2]};  
    assign ZCat[0] = Reg_File[3];  
endmodule
```

Constant Index

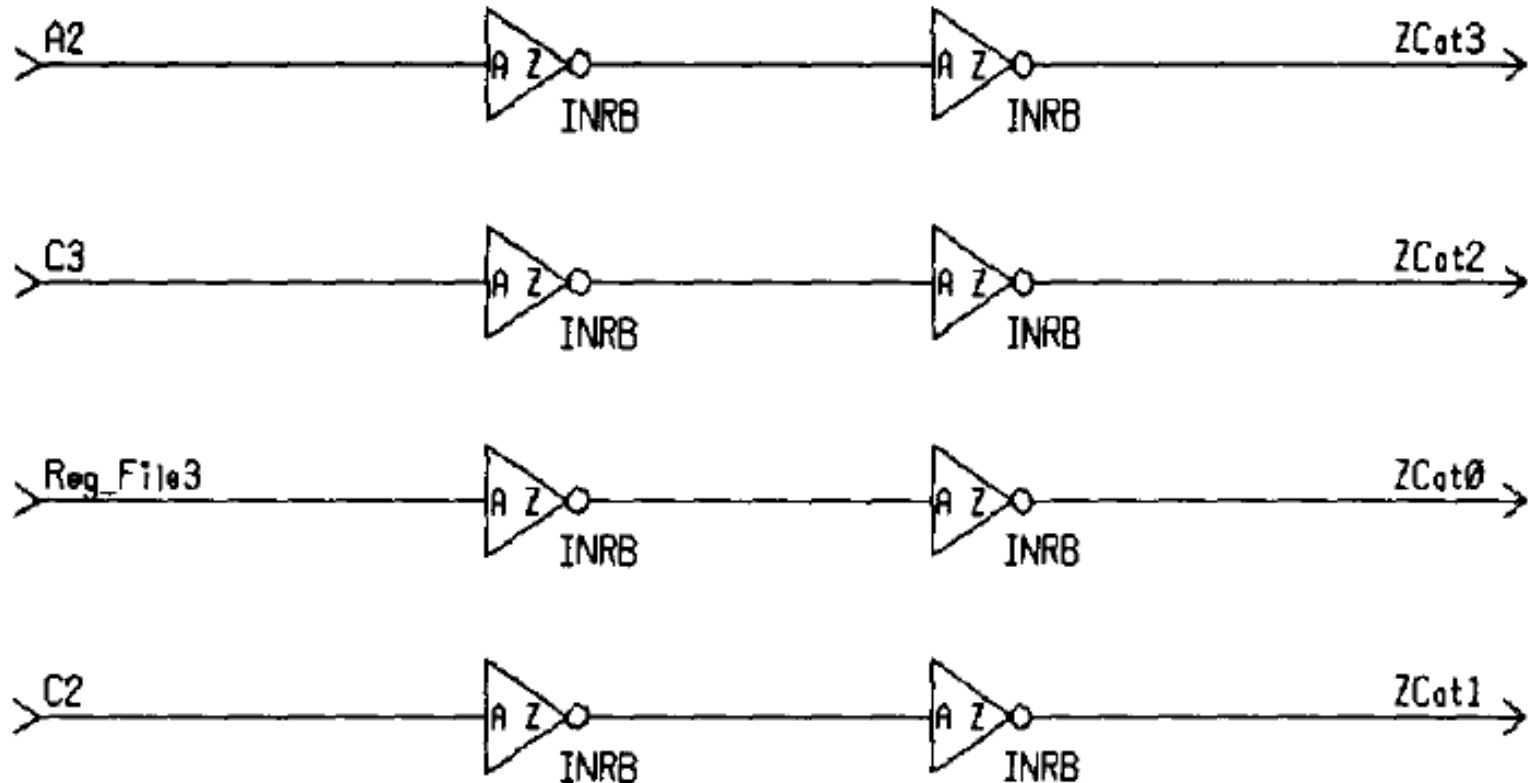


Constant bit-select.



Non-constant Index in Expression

```
module NonComputeRight (Data, Index, Dout);  
input [0:3] Data;  
input [1:2] Index;  
output Dout;  
    assign Dout = Data [Index];  
endmodule
```

Non-constant Index in Expression

 


Non-constant bit-select generates a multiplexer



Non-constant Index in Target

```
module NonComputeLeft (Mem, Store, Addr) ;  
output [7:0] Mem;  
input Store;  
input [1:3] Addr;  
    assign Mem [Addr] = Store;  
endmodule
```

Non-constant Index in Target

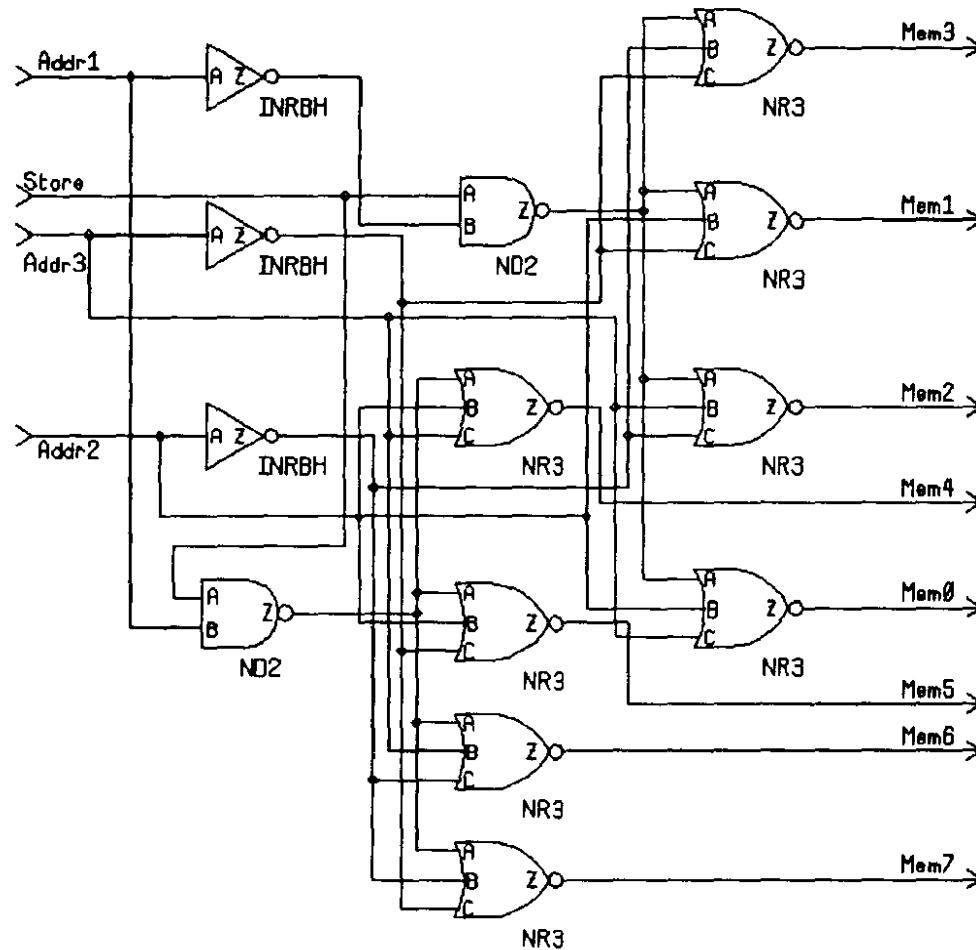

References

- Chapter 2, Verilog HDL Synthesis by J. Bhaskar
- Disclaimer: I don't own all the slides, these slides are copied and adopted from various publicly resources available on the internet.

Thank you