

# Advanced Digital System Design (EC6L033)

Verilog - Synthesis

Lecture 24: Logic Synthesis with Verilog HDL – Part7





---

# Objectives

- Blocking Vs Non-blocking

## Blocking Vs Non-blocking


- A single **Non-blocking** or **Blocking** assignment only inside an always block does not make a difference in the synthesis of the always block.
- If we mix both, then, there is a difference. Note the inputs to Flip-flop 2 and Flip-flop 3 ( See the example in the next slides).



# Blocking Vs Non-blocking

```
module FlagBits (ClockB, Strobe, Xflag, Mask,  
                | RightShift, SelectFirst, CheckStop);  
input ClockB, Strobe, Xflag, Mask;  
output RightShift, SelectFirst, CheckStop;  
reg RightShift, SelectFirst, CheckStop;  
  
always @ (negedge ClockB)  
    begin  
        RightShift = RightShift & Strobe; // Blocking  
        SelectFirst <= RightShift | Xflag; // Non-blocking  
        CheckStop <= SelectFirst ^ Mask; //Non-blocking  
    end  
endmodule
```

# Blocking Vs Non-blocking

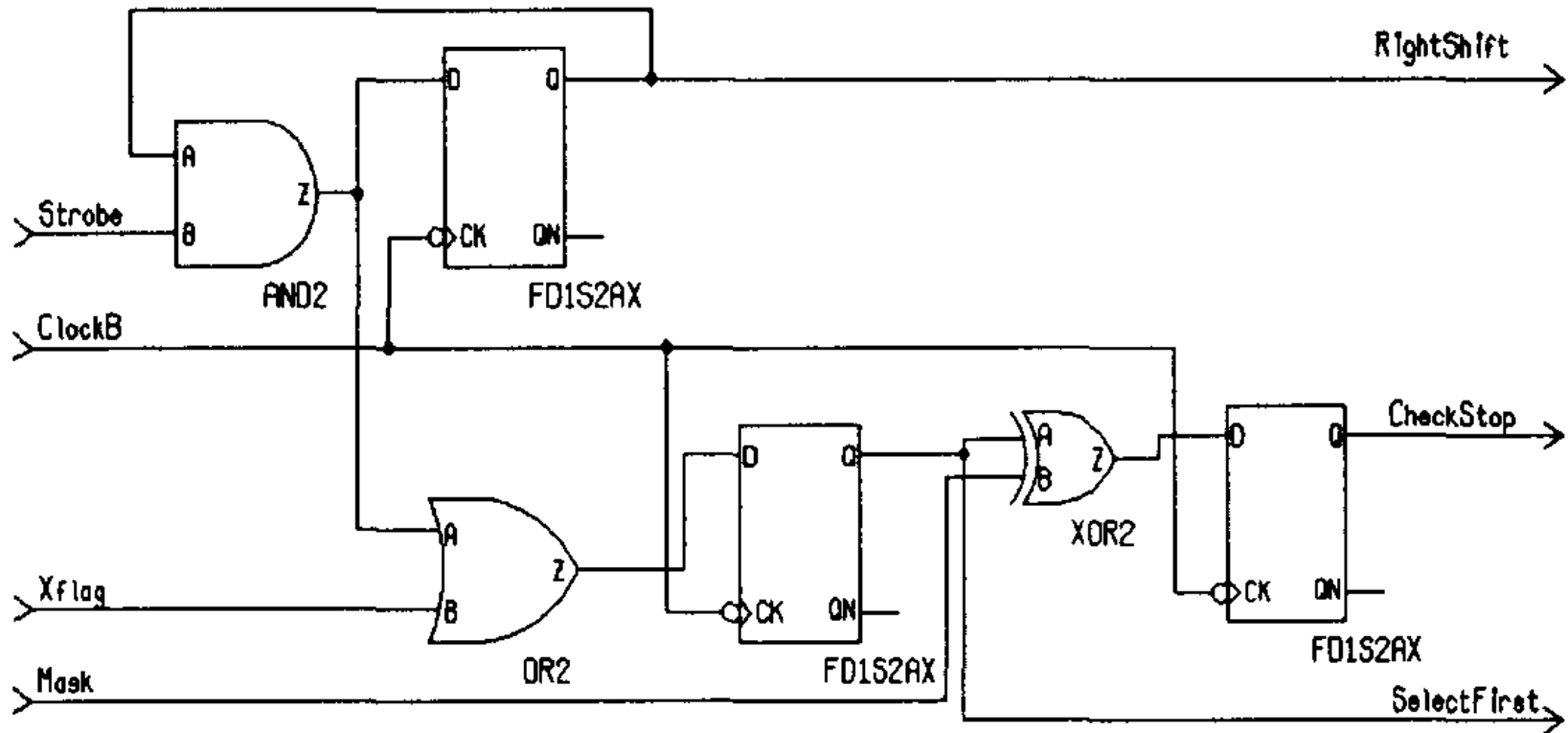

Non-blocking vs blocking procedural assignment.




# Blocking Vs Non-blocking

```
module NonBlockingExample (ClockZ, Merge, ER, Xmit,
                           FDDI, Claim);
input ClockZ, Merge, ER, Xmit, FDDI;
output Claim;
reg Claim;
reg FCR;

always @ (posedge ClockZ)
begin
    FCR <= ER | Xmit; // Assignment 1.
    if (Merge)
        Claim <= FCR & FDDI;
    else
        Claim <= FDDI; // Assignment 2.
end
endmodule
```

# Blocking Vs Non-blocking

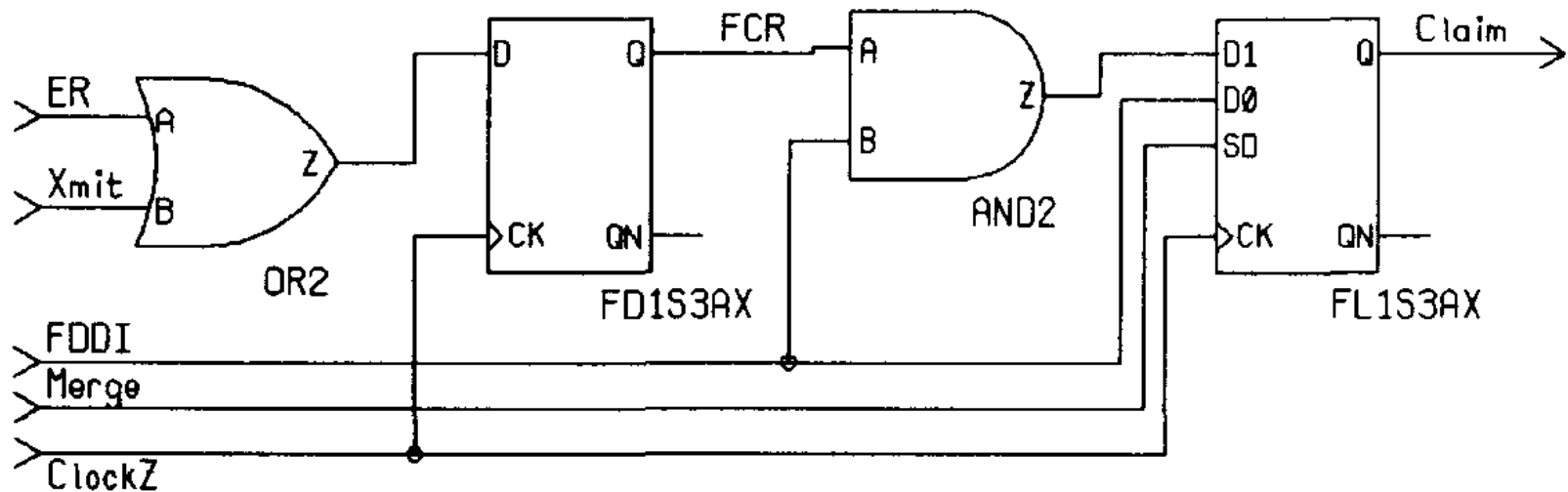


Non-blocking assignments.

# The Blocking Counterpart

```
module BlockingExample (ClockZ, Merge, ER, Xmit, FDDI, Claim);  
input ClockZ, Merge, ER, Xmit, FDDI;  
output Claim;  
reg Claim;  
reg FCR;  
  
always @ (posedge ClockZ)  
begin  
    FCR = ER | Xmit; // Assignment 1.  
    if (Merge)  
        Claim = FCR & FDDI; // Assignment 2.  
    else  
        Claim = FDDI;  
    end  
endmodule
```



# The Blocking Counterpart

 

Blocking assignments.

**Thank you**