

Digital Design with Verilog

Verilog - Synthesis

Lecture 18: Logic Synthesis with Verilog HDL – Part 1





Learning Objectives

- Mapping of few Verilog HDL types and constants to hardware
 - Reg data type
 - Constants
 - Parameters
- Value Holders for Hardware Modeling
 - Wire
 - Flip-Flop
 - Latch



Register Data Type

- The different kinds of register types that are supported for synthesis are:

`reg integer`

- A reg declaration explicitly specifies the size, that is, the corresponding number of bits of the variable in hardware.

```
reg [1:25] Cpt;    // 25-bit variable
reg Bxr;           // 1-bit variable
```

- When no size is explicitly specified in a reg declaration, the default is one bit.



Register Data Type

- For an integer type, the maximum size is 32 bits and the number is assumed to be in 2's complement form.
- Optionally a synthesis system may perform data flow analysis of the model to determine the maximum size of an integer variable. For example

```
wire [1:5] Brq, Rbu;  
integer Arb;  
...  
Arb = Brq + Rbu;
```



Register Data Type

- Size of *Arb* is determined to be 6 bits.
 - An adder of size 6 is sufficient.
 - The leftmost bit is the carry bit.
- The register types: time and real, are not supported for synthesis.

Constants

- There are three kinds of constants in Verilog HDL: integer, real and string.
- Real and string constants are not supported for synthesis.
- An integer constant can be written in either of the following two forms.
 - Simple decimal
 - Base format



Constants

- If an integer is written in the base format form, then the integer is treated as an unsigned number.
- If a size is explicitly specified for the integer, then the specified size is the number of bits used for the integer; if not, 32bits is used for the size.

30	Signed number, 32 bits
-2	Signed number, 32 bits in 2 's complement
2'b10	Size of 2 bits
6'd-4	6-bit unsigned number (-4 is represented in 2's complement using 6 bits)
'd-10	32-bit unsigned number (-10 is represented in 2's complement using 32 bits)



Parameters

- A parameter is a named constant. Since no size is allowed to be specified for a parameter, the size of the parameter is the same as the size of the constant itself.

```
parameter RED = -1 , GREEN = 2 ;  
parameter READY= 2'b01, BUSY= 2'b11, EXIT= 2'b10;
```

- *RED* and *GREEN* are two 32-bit signed constants. *READY*, *BUSY* and *EXIT* are three parameters of size 2 bits each.



Value Holders for Hardware Modeling

- The basic value holders in hardware are:
 - Wire
 - Flip-flop (an edge-triggered storage element)
 - Latch (a level-sensitive storage element)
- A variable in Verilog HDL can either be of the net data type or the register data type.
- For synthesis, a variable of net type maps to a wire in hardware and a variable of the register type maps either to a wire or a storage element (flip-flop or latch) depending on the context under which the variable is assigned a value



Value Holders for Hardware Modeling

- In Verilog HDL, a **register** variable retains its value through the entire simulation run, thus may infer memory.
 - However, this is too general for synthesis.
- Here is an example of a variable that is used as a temporary and therefore need not be a candidate for a storage element.




Value Holders for Hardware Modeling

```
wire Acr, Bar, Fra;  //A wire is a net type.
reg Trq, Sqp;  //A reg is a register type.
...
always @ (Bar or Acr or Fra)
begin
Trq = Bar & Acr;
Sqp = Trq | Fra;
end
```

- Variable *Trq* is assigned in the first statement and then used in the right hand- side expression of the second statement.
- Verilog HDL semantics indicate that *Trq* retains its value through the entire simulation run.

Value Holders for Hardware Modeling

 
- However, it is not necessary to store the value of Trq as a storage element in hardware, since it is assigned and used immediately.



Variable Trq is a wire.

Value Holders for Hardware Modeling

```
wire Acr, Bar, Fra;  
reg Trq, Sqp;  
...  
always @ (Bar or Acr or Fra)  
begin  
    Sqp = Trq | Fra;  
    Trq = Bar & Acr;  
end
```

 


No latch for variable *Trq*.



Value Holders for Hardware Modeling
 
```
wire Sat, Ant;  
reg Fox, Sout;  
...  
always @ (Sat or Ant)  
begin  
  if (!Sat)  
    Fox = Ant;  
  Sout = ! Fox;  
end
```



FD1S1A

Variable *Fox* is a latch

Verilog Constructs to Gates



Objectives

- Synthesis of Verilog Constructs
 - Procedural Assignment statements
- Blocking Vs Non Blocking
- Assignment restrictions for synthesis




Continuous Assignment

- This represents in hardware, logic that is derived from the expression on the right-hand-side of the assignment statement driving the net that appears on the left-hand-side of the assignment statement.
- The target of a continuous assign statement is always a net driven by combinational logic.

```
module Continuous (Statin, StatOut);  
    input Statin;  
    output Statout;  
    assign Statout= ~Statin;  
endmodule
```

The Synthesized circuit

 

Delays in continuous assignments are ignored by the synthesis tool.

assign #2 EffectiveAB = DriverA | DriverB;

The #2 delay is ignored



Procedural Assignment Statement

- Two types
 - Blocking
 - Non-blocking
- In hardware, logic that is derived from the expression on the right-hand-side of the assignment statement drives the variable that appears on the left-hand-side of the assignment.



Procedural Assignments

- Procedural assignments can appear within an 'initial' or 'always' block; however, an 'initial' block is not supported for synthesis.
- **We consider procedural assignments only inside a 'always' block.**



Blocking procedural assignment

```
module Blocking (Preset, Count);  
    input [0:2] Preset;  
    output [3:0] Count;  
  
    reg[3:0] Count;  
  
    always @(Preset) //Adder with 1 and Preset as  
        Count = Preset + 1; //Inputs  
endmodule
```

- A 3-bit adder is costly –so we optimize.



The Optimization

pre0	pre1	pre2	Cou3	Cou2	Cou1	Cou0
0	0	0	0	0	0	1
0	0	1	0	0	1	0
0	1	0	0	0	1	1
0	1	1	0	1	0	0
1	0	0	0	1	0	1
1	0	1	0	1	1	0
1	1	0	0	1	1	1
1	1	1	1	0	0	0



The equations


```
Count0 = !Preset2;  
Count1 = (!Preset1 & Preset2) | (Preset1 & !Preset2)  
Count2 = Preset0 & (!Preset1 | !Preset2) |  
          (!Preset0 & Preset1 & Preset2)  
Count3 = Preset0 & Preset1 & Preset2;
```

- We use Demorgan's law

$$\overline{A} \overline{B} + \overline{C} \overline{D} = \overline{(A + B) (C + D)}$$

- OR –AND –INVERT construct
- See Slide for the circuit

Implemented Circuit




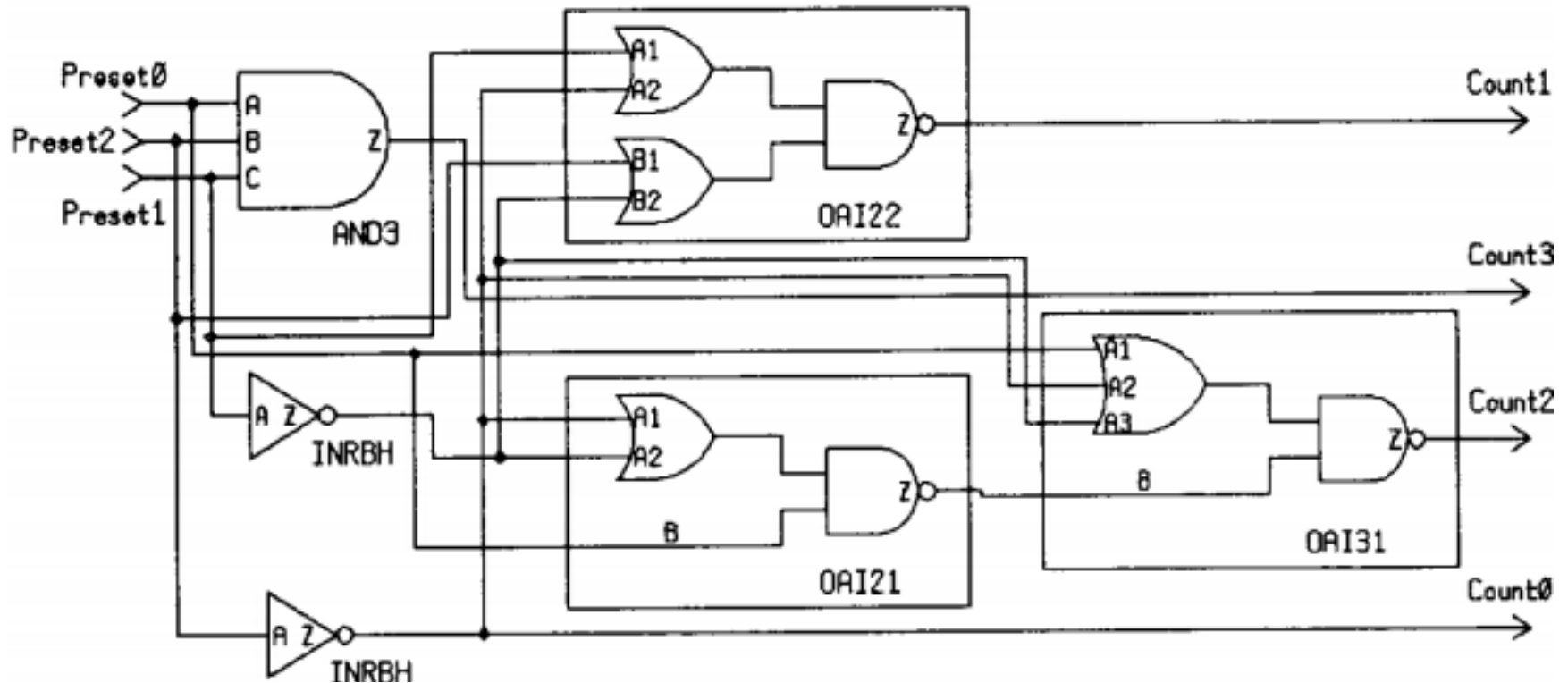




Non-Blocking Procedural Assignment

```
module NonBlocking(RegA, Mask, RegB);  
    input [3:0] RegA, Mask;  
    output [3:0] RegB;  
  
    reg[3:0] RegB;  
    always @(RegA or Mask)  
        RegB<= RegA& Mask;  
  
endmodule
```

The Circuit

    



The Synthesis part

- Blocking or Non-blocking does not change the resultant combinational logic.
- Tips: Use Blocking assignments for modeling combinational logic and non-blocking assignments for modeling sequential logic.
- Why? –wait for some more time 😊))




Target of Assignment

- Target of a procedural assignment is synthesized to a **wire**, a **flip-flop**, or a **latch**, depending on the context.
- If the assignment is under the control of an edge of a clock, it infers a flip-flop.

```
module Target(Clk, RegA, RegB, Mask);  
    input Clk;  
    input [3:0] RegA, Mask;  
    output [3:0] RegB;  
  
    reg[3:0] RegB;  
  
    always @(posedgeClk)  
        RegB<= RegA& Mask;  
  
endmodule
```

The Circuit

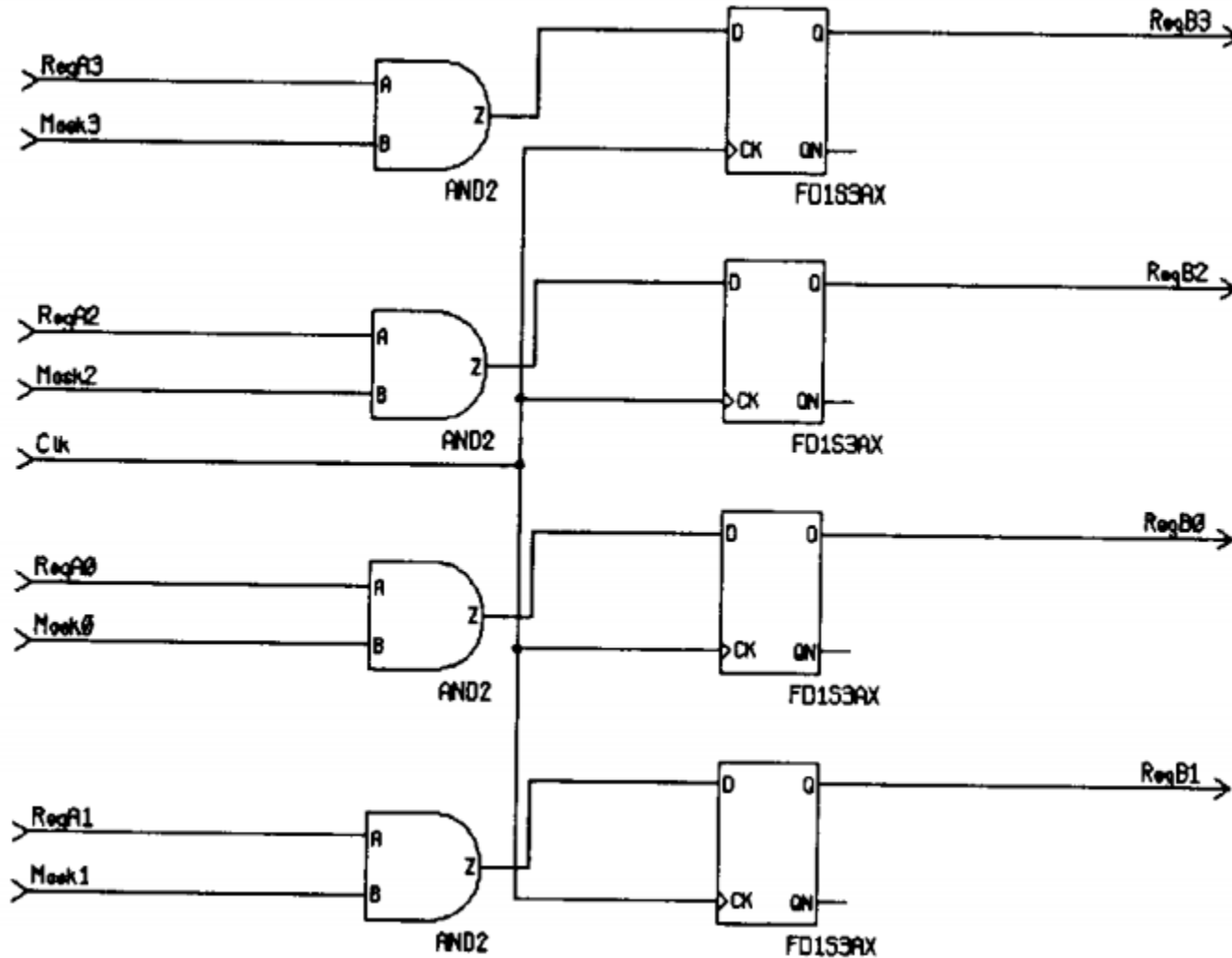



Assignment Restrictions

- Any kind of delay control is ignored. This can basically lead to a mismatch between the Verilog and Synthesized modules.

```
#5 RegB<= RegA& Mask;  
RegB= #2 RegA& Mask;
```

- Rule: A target cannot be assigned using a blocking assignment and a non-blocking assignment.



Explaining the Rule.

- If a target is assigned using a blocking (or a non-blocking) assignment, then the same target can only be assigned again using a blocking (or a non-blocking) assignment.

```
Count = Preset + 1;  
Count <= Mask; //This is illegal since count is  
//previously assigned using a blocking assignment
```



References

- Chapter 1 & 2, Verilog HDL Synthesis by J. Bhaskar
- Disclaimer: I don't own all the slides, these slides are copied and adopted from various public resources available on the internet.

Thank you